

EEE-2103: Electronic Devices and Circuits

Dept. of Computer Science and Engineering
University of Dhaka

Prof. Sazzad M.S. Imran, PhD
Dept. of Electrical and Electronic Engineering
sazzadmsi.webnode.com

Coupling and Bypassing Capacitor


dc bias voltage $V_B = \frac{V_{CC} \times R_2}{R_1 + R_2}$

Signal source directly connected to circuit →
bias voltage is altered to $V_B = \frac{V_{CC} \times (r_s \parallel R_2)}{R_1 + (r_s \parallel R_2)}$

C_1 is open-circuit to dc →
 r_s does not effect V_B

C_1 is short-circuit for ac →
 v_s appears at transistor base

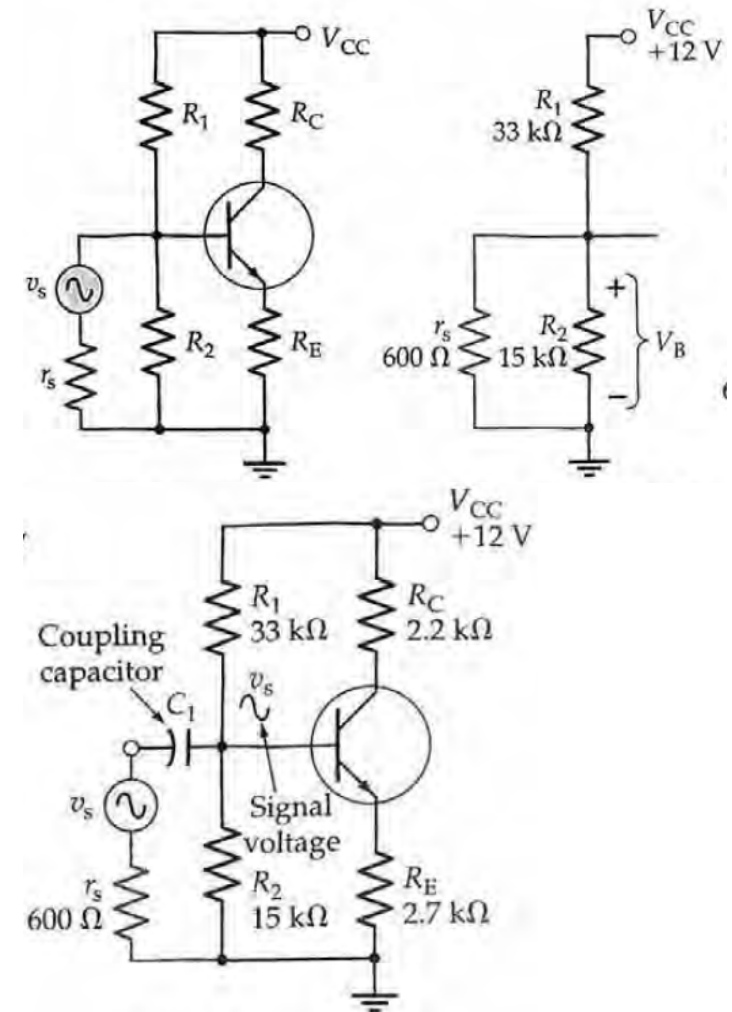Signal is ac-coupled to circuit input →
 C_1 is called input coupling capacitor




Coupling and Bypassing Capacitor

Directly coupling R_L to circuit output \rightarrow
 supply voltage is reduced to $V = \frac{V_{CC} \times R_L}{R_C + R_L}$
 collector resistance becomes $R = R_C || R_L$

C_2 is open-circuit to dc +
 C_2 is short-circuit for ac \rightarrow
 passes ac output waveform to load
 does not affect dc bias condition

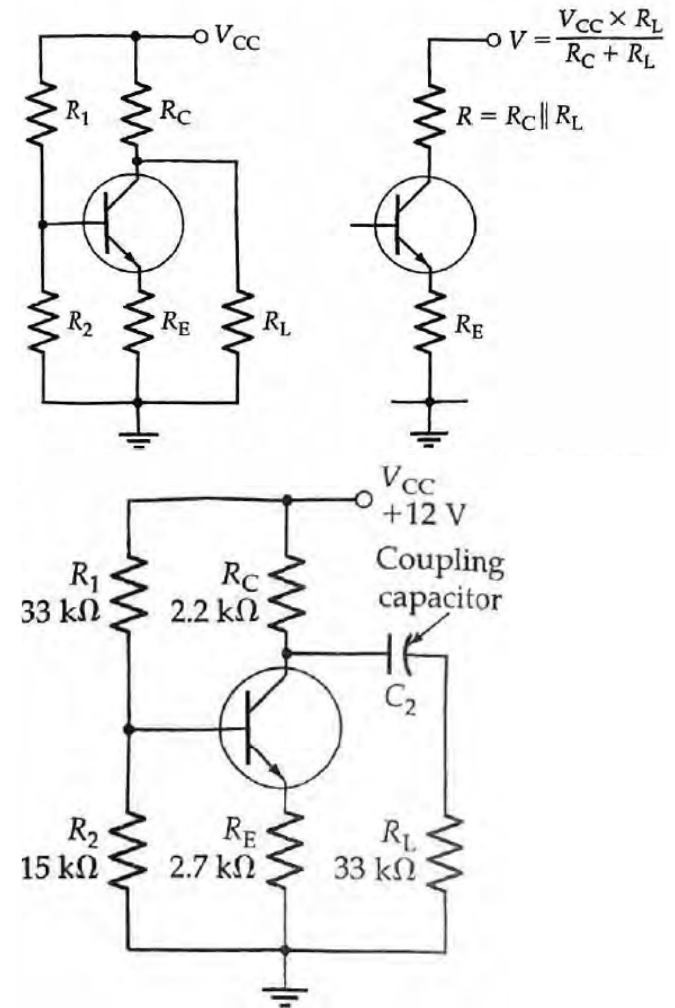Signal is ac-coupled to circuit output \rightarrow
 C_2 is called output coupling capacitor



Coupling and Bypassing Capacitor

Emitter bypassing:

Without $C_E \rightarrow$

R_E provides negative feedback to stabilize Q -point

R_E opposes variation in I_E

change in V_{CE} is fed back to base = I_B changes

ac signal sees $r_e + R_E \rightarrow$ ac gain decreases


With $C_E \rightarrow$

C_E provides ac short circuit across R_E

removes ac feedback

ac gain increases

C_E is called emitter bypass capacitor

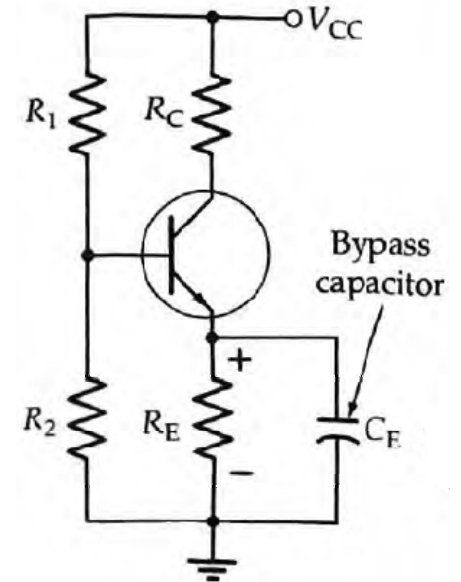

AC Load Lines

AC equivalent circuits:

Capacitors behave short-circuits to ac signals →
all capacitors replaced with short circuits.



ac signals do not affect dc supply voltage →
power supply behaves as ac short-circuit
replace power supply by short circuit.

AC load lines:

Represent ac performance of circuit.

$$\text{dc load} = R_C + R_E$$

$$\text{ac load} = R_C || R_L$$

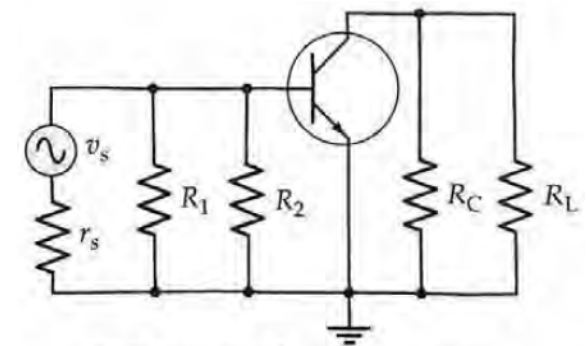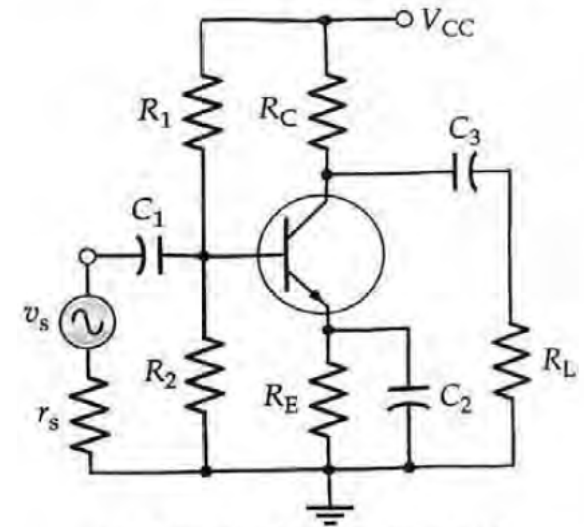

AC Load Lines

AC load lines:

No input signal \rightarrow

voltage and current condition = Q -point on dc load line

ac input signal \rightarrow

voltage and current vary above and below Q -point



Q -point is common to both dc and ac load lines

Convenient I_C change $\rightarrow \Delta I_C = I_{CQ}$

Calculate corresponding V_{CE} change = ΔV_{CE}

Point $C = (V_{CEQ} + \Delta V_{CE}, I_{CQ} - \Delta I_C)$

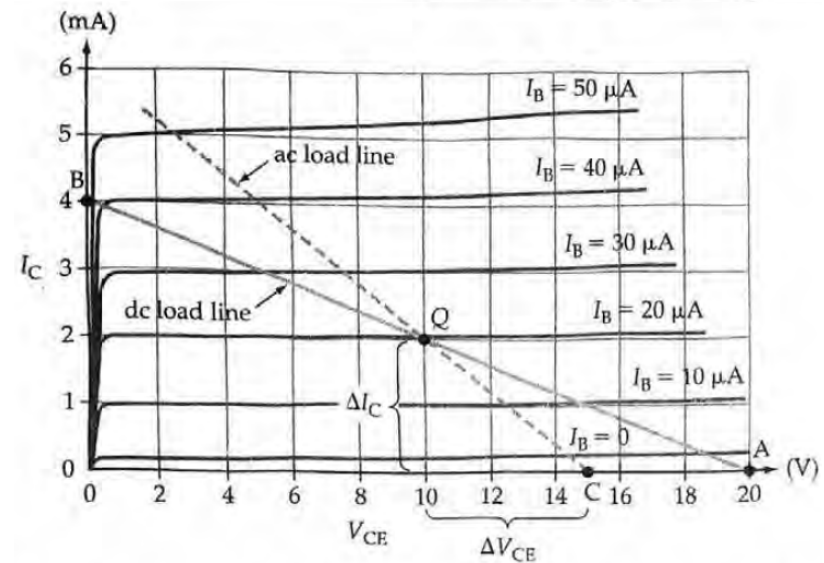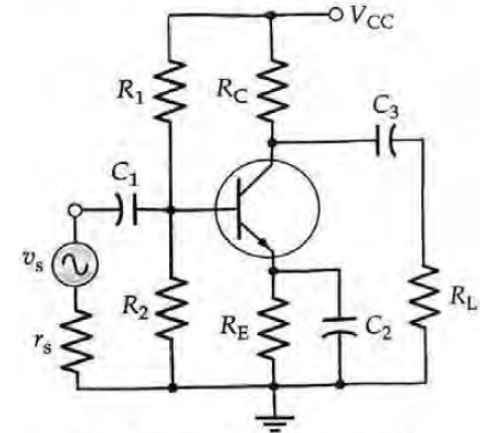ac load line = line through points C and Q .



AC Load Lines

Problem-31:

Draw the dc and ac load lines for the transistor circuit in Fig. 31(a), using the transistor common-emitter characteristics in Fig. 31(b).

Drawing dc load line \rightarrow

$$R_{L(dc)} = R_C + R_E = 2.2 \times 10^3 + 2.7 \times 10^3 = 4.9 \text{ k}\Omega$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$



$$I_C = 0 \rightarrow V_{CE} = V_{CC} = 20 \text{ V}$$

Point A = (20 V, 0)

$$V_{CE} = 0 \rightarrow I_C = V_{CC}/(R_C + R_E) = 20/4.9 \times 10^3 = 4.08 \text{ mA}$$

Point B = (0, 4.08 mA)

Draw dc load line through A and B.

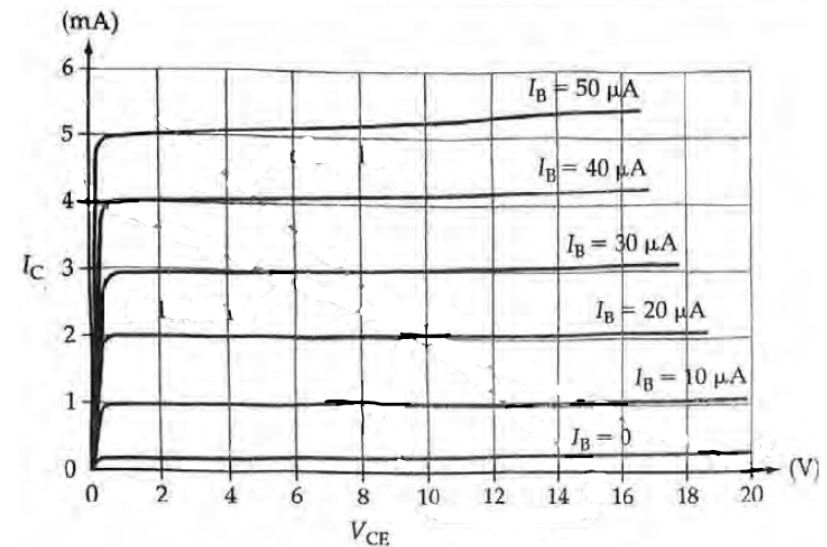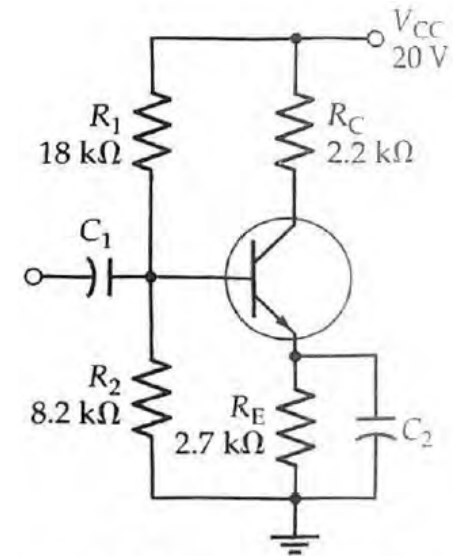

AC Load Lines

Problem-31:

$$V_B = \frac{V_{CC} \times R_2}{R_1 + R_2} = \frac{20 \times 8.2 \times 10^3}{18 \times 10^3 + 8.2 \times 10^3} = 6.3 \text{ V}$$

$$V_E = V_B - V_{BE} = 6.3 - 0.7 = 5.6 \text{ V}$$

$$I_C \approx I_E = V_E / R_E = 5.6 / 2.7 \times 10^3 = 2.07 \text{ mA}$$

Mark Q -point on dc load line at $I_C = 2.07 \text{ mA}$

Drawing ac load line \rightarrow

$$R_{L(ac)} = R_C = 2.2 \text{ k}\Omega$$

I_C changes by $\Delta I_C = I_{CQ} = 2.07 \text{ mA} \rightarrow$

$$\Delta V_{CE} = \Delta I_C \times R_C = 2.07 \times 10^{-3} \times 2.2 \times 10^3 = 4.55 \text{ V}$$

Point $C = (V_{CEQ} + \Delta V_{CE}, I_{CQ} - \Delta I_C)$

$$= (10 + 4.55, 2.07 - 2.07) = (14.55, 0)$$

Draw ac load line through points C and Q .

