

# **EEE-2103: Electronic Devices and Circuits**

Dept. of Computer Science and Engineering  
University of Dhaka

Prof. Sazzad M.S. Imran, PhD  
Dept. of Electrical and Electronic Engineering  
[sazzadmsi.webnode.com](http://sazzadmsi.webnode.com)

# Half-Wave Rectifier Power Supply

Capacitor filter circuit:

Smoothing circuit or filter →

to convert series of +ve/-ve half-cycles to dc voltage.





When  $D_1$  is forward biased,  $C_1$  is charged to Peak capacitor voltage →

$$V_C = V_{pi} - V_F$$

When  $D_1$  is reverse biased,  $C_1$  is discharged slowly through  $R_L$ .

Charge and discharge of  $C_1$  cause small increase and decrease in  $V_C =$

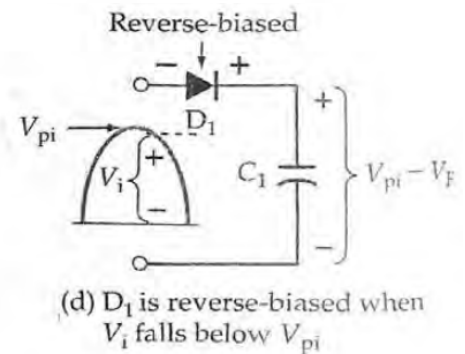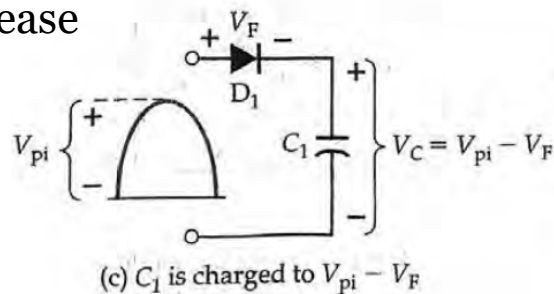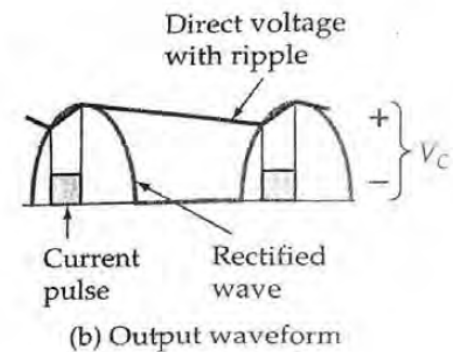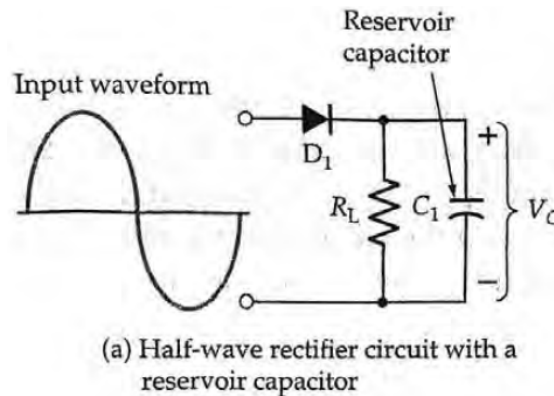Output is direct voltage with small ripple.



# Half-Wave Rectifier Power Supply

Quantities of circuit output voltage waveform →

$E_{o(ave)}$  = average dc output voltage

$E_{o(max)}$  = maximum output voltage

$E_{o(min)}$  = minimum output voltage

$V_r$  = ripple voltage peak-to-peak amplitude

$T$  = time period of ac input waveform

$t_1$  = capacitor discharge time

$t_2$  = capacitor charge time

$\theta_1$  = phase angle of input wave from zero to  $E_{o(min)}$


$\theta_2$  = phase angle of input wave from  $E_{o(min)}$  to  $E_{o(max)}$

Assumption →  $t_1 \gg t_2$

Reservoir capacitor value →

$$C_1 = I_L t_1 / V_r$$

$I_L$  = load current

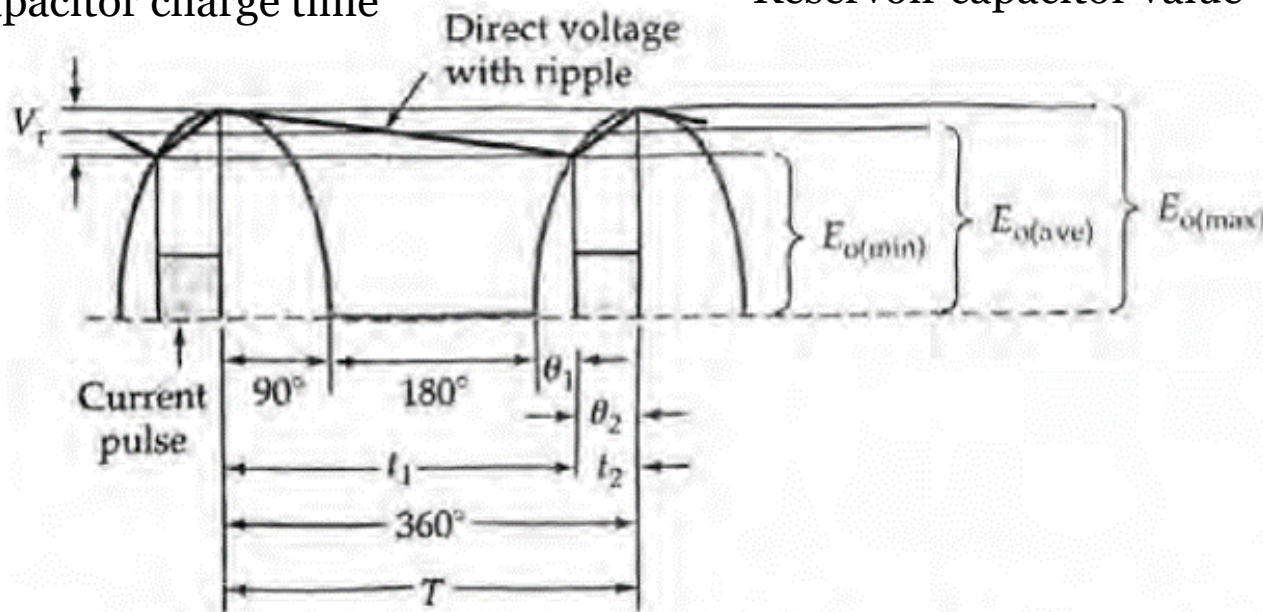

# Half-Wave Rectifier Power Supply

## Problem-7:


Determine the peak-to-peak ripple voltage for a half-wave rectifier and filter circuit which has a  $680\ \mu\text{F}$  reservoir capacitor, an average output of  $28\ \text{V}$ , and a  $200\ \Omega$  load resistance. Frequency of the ac input waveform is assumed to be  $60\ \text{Hz}$ .

Load current,  $I_L = E_{o(ave)}/R_L = 28/200 = 140\ \text{mA}$


Time period of ac input waveform,  $T = 1/f = 1/60 = 16.7\ \text{ms}$

Capacitor discharge time,  $t_1 \approx T = 16.7\ \text{ms}$

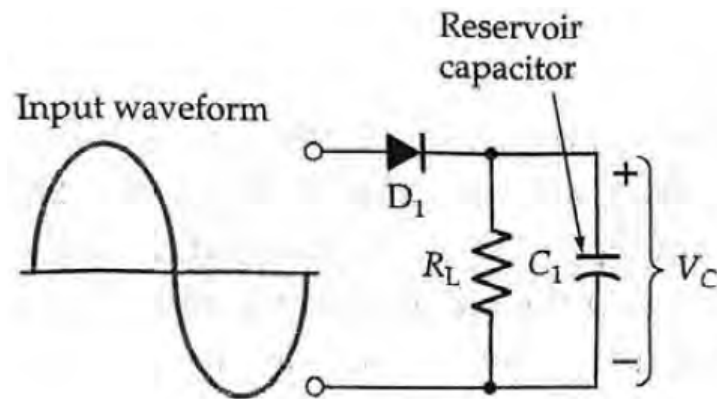Peak-to-peak ripple voltage,  $V_r = I_L t_1 / C_1 = (140 \times 10^{-3} \times 16.7 \times 10^{-3}) / 680 \times 10^{-6} \approx 3.4\ \text{V}$



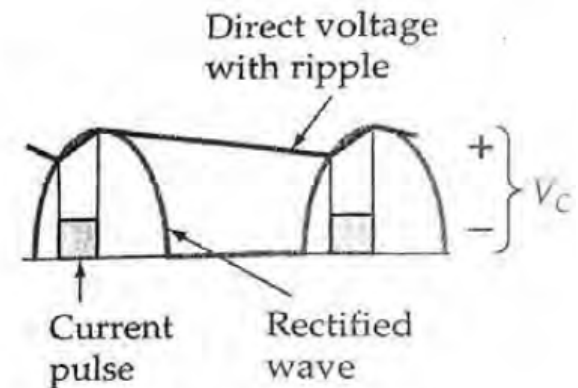(a) Half-wave rectifier circuit with a reservoir capacitor



(b) Output waveform

# Half-Wave Rectifier Power Supply

## Problem-8:

A half-wave rectifier dc power supply is to provide 20 V to a 500  $\Omega$  load as shown in Fig. 8. The peak-to-peak ripple voltage is not to exceed 10% of the average output voltage, and the ac input frequency is 60 Hz. Calculate the required reservoir capacitance.

Time period of ac input waveform,  $T = 1/f = 1/60 = 16.7$  ms


Capacitor discharge time,  $t_1 \approx T = 16.7$  ms

Peak-to-peak ripple voltage,  $V_r = 10\%$  of  $E_{o(ave)}$   
 $= 20 \times 10 / 100 = 2$  V

Load current,  $I_L = E_{o(ave)} / R_L = 20 / 500 = 40$  mA

Reservoir capacitor value
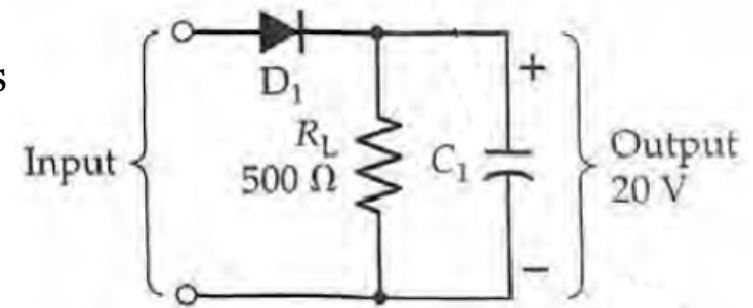
$$C_1 = I_L t_1 / V_r = (40 \times 10^{-3} \times 16.7 \times 10^{-3}) / 2 \\ = 334 \mu\text{F (use 330 } \mu\text{F standard value)}$$



# Full-Wave Rectifier Power Supply

Convert output waveform to dc voltage.

Reservoir capacitor smooth output voltage.

Surge-limiting resistor protects diodes.

Reservoir capacitance,  $C_1 = I_L t_1 / V_r$


Repetitive current,  $I_{FRM} = I_L(t_1 + t_2) / t_2$

Each pair of diodes conducts during alternate half-cycle.

Average forward current for each diode,  $I_{F(ave)} = I_L / 2$

Assumption  $\rightarrow t_1 \gg t_2$

$t_1 = T/2 - t_2 \approx T/2$

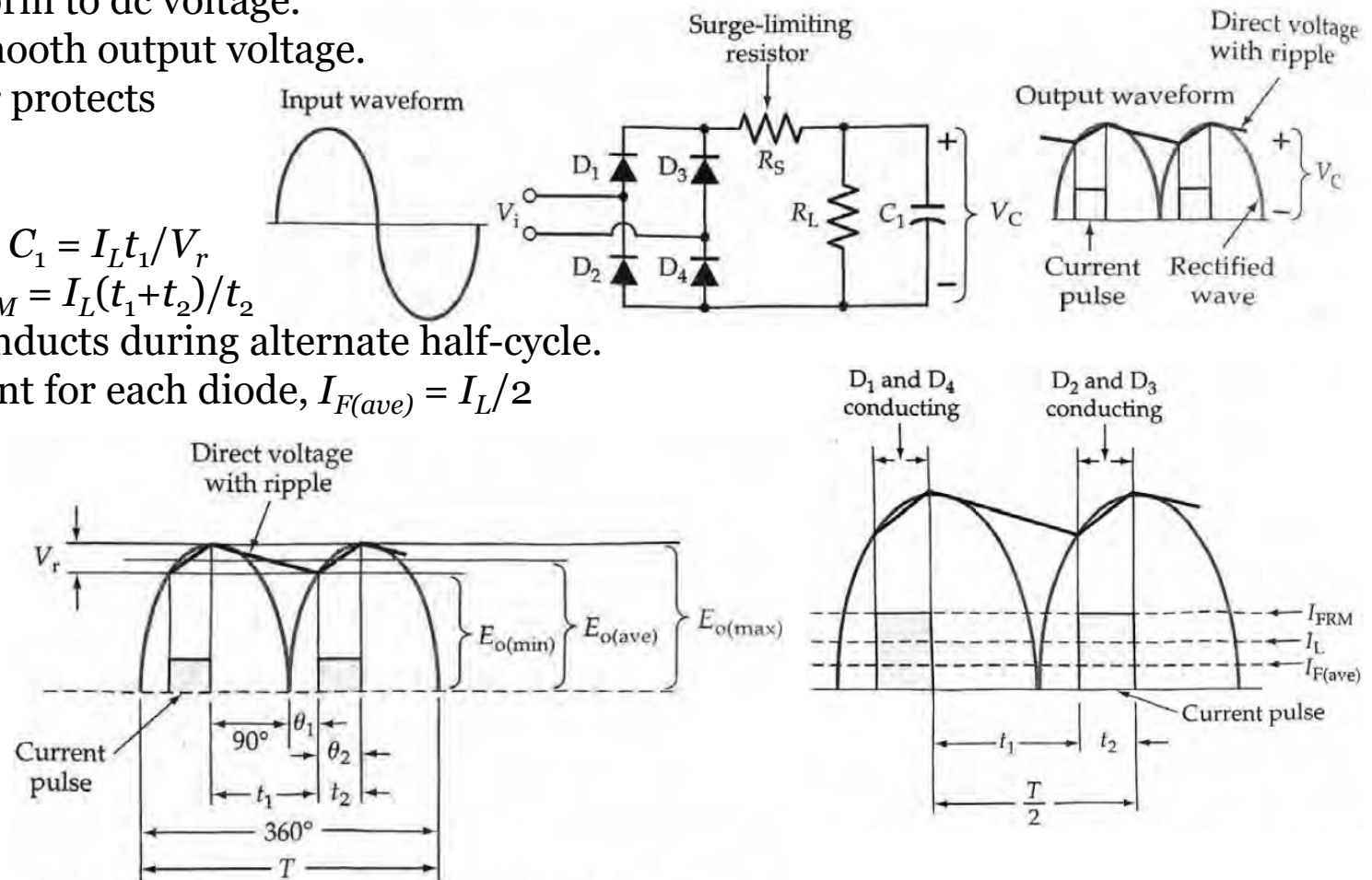

# Full-Wave Rectifier Power Supply

## Problem-9:

The full-wave rectifier dc power supply in Fig. 9 is to supply 20 V to a 500  $\Omega$  load. The peak-to-peak ripple voltage is not to exceed 10% of the average output voltage, and the ac input frequency is 60 Hz. Calculate the required reservoir capacitor value.

Time period of ac input waveform,  $T = 1/f = 1/60 = 16.7$  ms

Capacitor discharge time,  $t_1 \approx T/2 = 16.7/2 = 8.35$  ms

Peak-to-peak ripple voltage,  $V_r = 10\%$  of  $E_{o(ave)}$   
 $= 20 \times 10/100 = 2$  V

Load current,  $I_L = E_{o(ave)}/R_L = 20/500 = 40$  mA

Reservoir capacitor value

$$C_1 = I_L t_1 / V_r = (40 \times 10^{-3} \times 8.35 \times 10^{-3}) / 2$$

$$= 167 \mu\text{F} \text{ (use } 150 \mu\text{F standard value)}$$

