

EEE-2103: Electronic Devices and Circuits

Dept. of Computer Science and Engineering
University of Dhaka

Prof. Sazzad M.S. Imran, PhD
Dept. of Electrical and Electronic Engineering
sazzadmsi.webnode.com

Common Emitter Circuit Analysis




Capacitors are ac short circuits →

input terminals are base-emitter.

output terminals are collector-emitter.



180° phase shift between input and output waveforms.

Input impedance and output impedance →

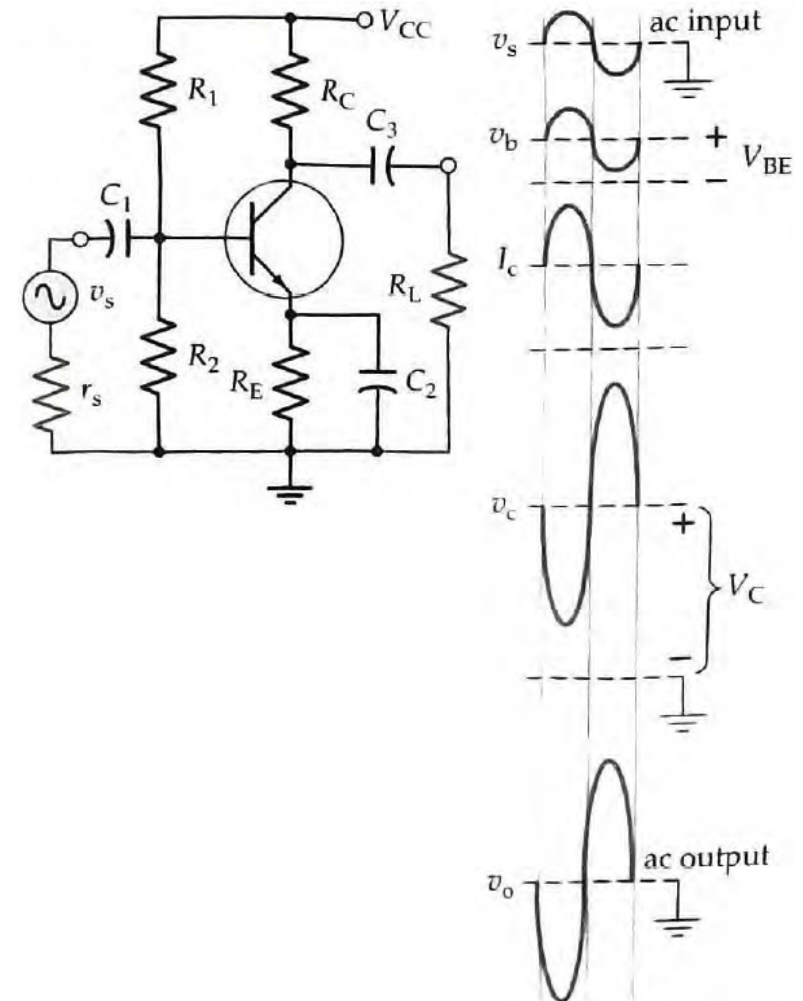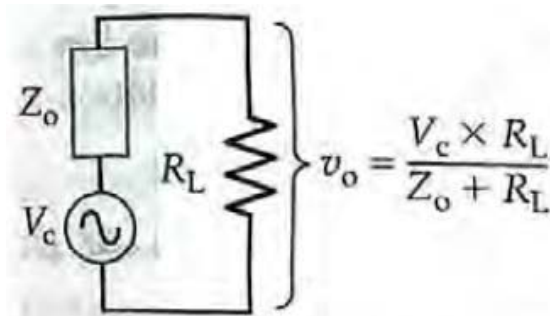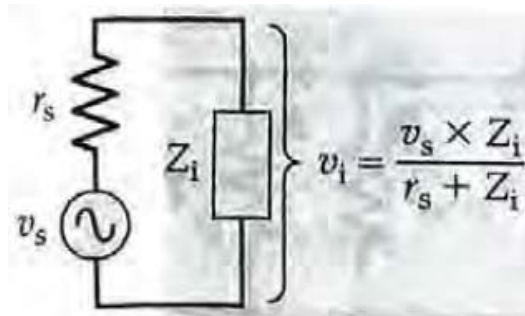


Common Emitter Circuit Analysis

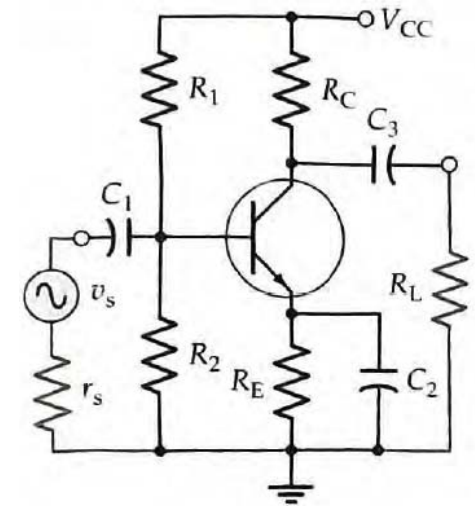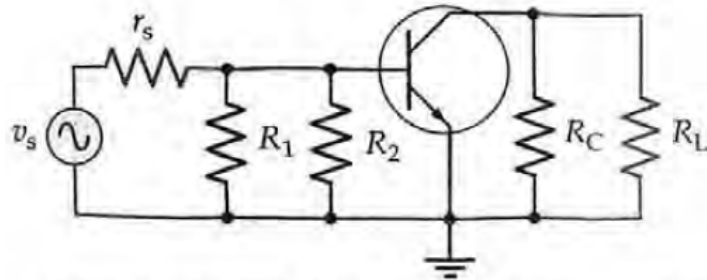ac equivalent circuit →
power supply and capacitors = short circuit.



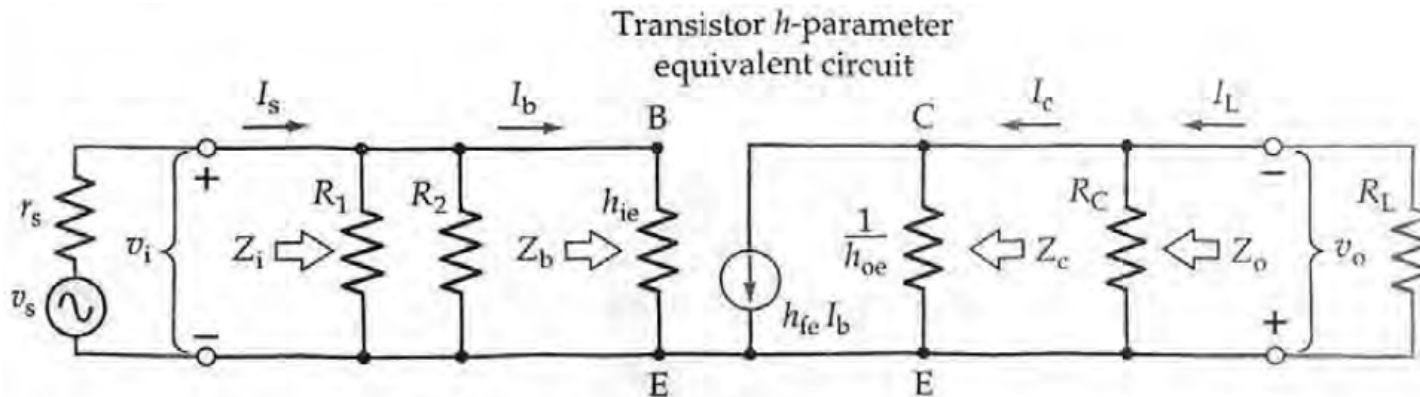h -parameter circuit →
replace transistor with its h -parameter model



Common Emitter Circuit Analysis

Input impedance at base terminal \rightarrow

$$Z_b \approx h_{ie} \approx 1.5 \text{ k}\Omega$$

Circuit input impedance \rightarrow




$$Z_i = R_1 || R_2 || h_{ie}$$

Output impedance at collector terminal \rightarrow

$$Z_c \approx 1/h_{oe} \approx 50 \text{ k}\Omega$$

Circuit output impedance \rightarrow

$$Z_o \approx R_c || (1/h_{oe})$$

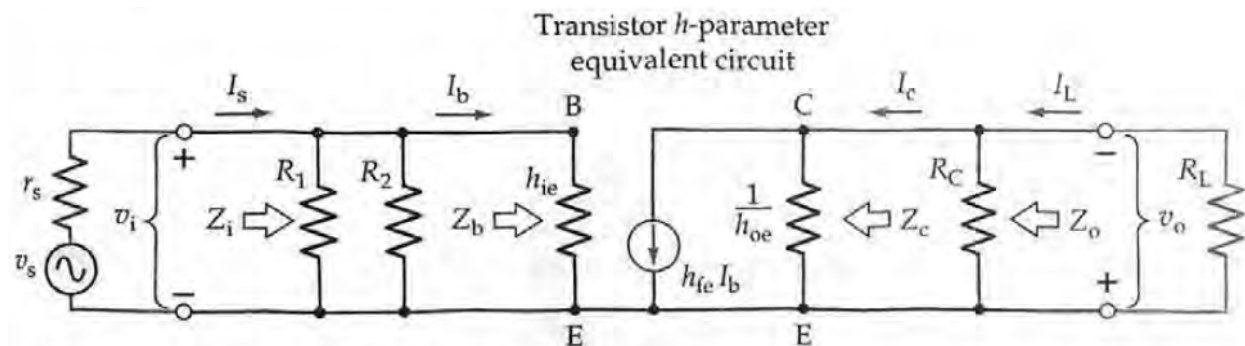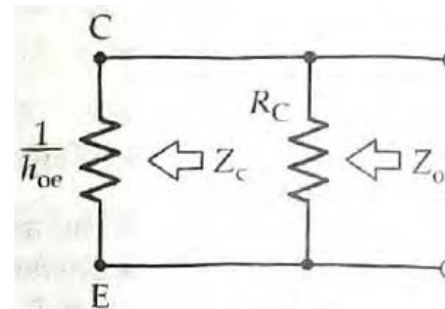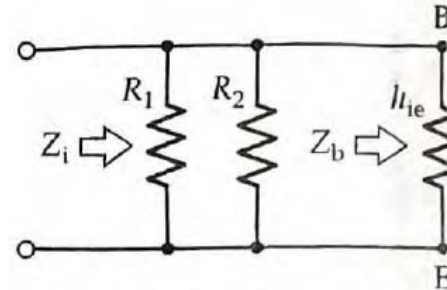

Common Emitter Circuit Analysis

Voltage gain \rightarrow

$$A_v = v_o / v_i$$


$$v_i = I_b h_{ie}$$

$$v_o = -I_c (R_C \parallel R_L)$$


$$A_v = \frac{-I_c (R_C \parallel R_L)}{I_b h_{ie}} = \frac{-h_{fe} (R_C \parallel R_L)}{h_{ie}}$$

$$A_v \approx \frac{-(R_C \parallel R_L)}{h_{ib}}$$

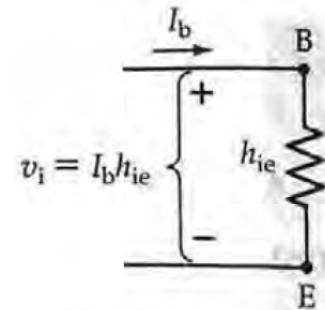
Minus sign = v_o is 180° out of phase with v_i



(a) Input voltage

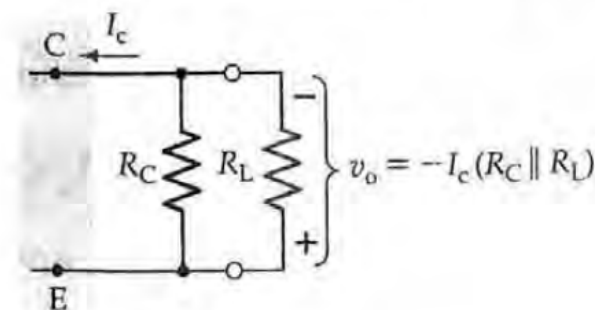

(b) Output voltage

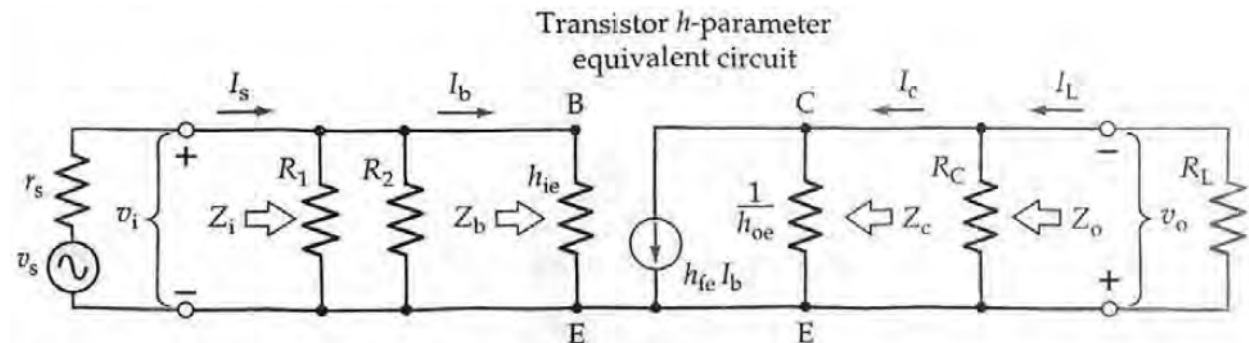

Common Emitter Circuit Analysis

Current gain →

Device current gain (not circuit gain) =

$$h_{fe} = I_c / I_b$$

Signal current $I_s \rightarrow h_{ie}$ and $R_B = R_1 || R_2$


Output current $I_c \rightarrow R_C$ and R_L

Circuit current gain →

$$A_i = \frac{h_{fe} R_C R_B}{(R_C + R_L)(R_C + h_{ie})}$$

Power gain →

$$A_p = A_v \times A_i$$

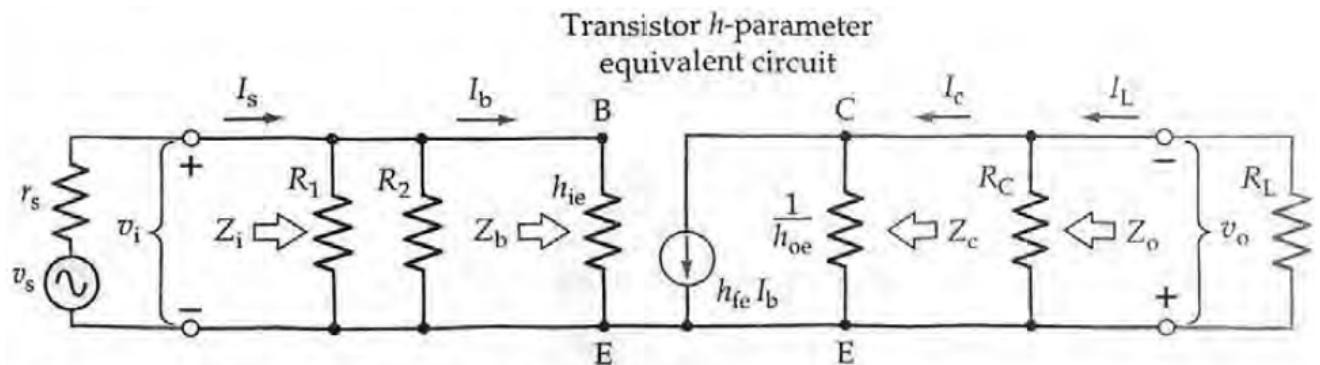

Common Emitter Circuit Analysis

Problem-32:

The transistor in the CE circuit in Fig. 32 has the following parameters: $h_{ie} = 2.1 \text{ k}\Omega$, $h_{fe} = 75$, and $h_{oe} = 1 \text{ }\mu\text{S}$. Calculate the circuit input impedance, output impedance, and voltage gain.

Input impedance \rightarrow


$$Z_i = R_1 || R_2 || h_{ie} = 68 || 56 || 2.1 \text{ k}\Omega = 1.97 \text{ k}\Omega$$

Output impedance \rightarrow

$$Z_o \approx R_C || (1/h_{oe}) = 3.9 \times 10^3 || [1/(1 \times 10^{-6})] \approx 3.9 \text{ k}\Omega$$

Voltage gain \rightarrow

$$A_v = \frac{-h_{fe}(R_C || R_L)}{h_{ie}} = \frac{-75 \times (3.9 \times 10^3 || 82 \times 10^3)}{2.1 \times 10^3} = -133$$

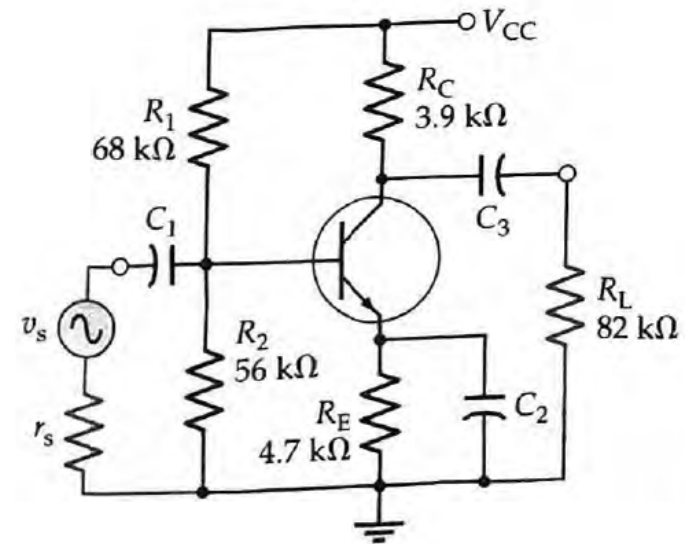

Common Emitter Circuit Analysis

Problem-33:

The transistor in the CE circuit in Fig. 33 has the following parameters: $h_{ie} = 2.1 \text{ k}\Omega$, $h_{fe} = 75$, and $h_{oe} = 1 \text{ }\mu\text{S}$. Calculate the circuit input impedance, output impedance, and voltage gain.

$$\begin{aligned} Z_b &= h_{ie} + R_E(1+h_{fe}) = 2.1 \times 10^3 + 4.7 \times 10^3(1+75) \\ &= 359 \text{ k}\Omega \end{aligned}$$

Input impedance \rightarrow


$$Z_i = R_1 || R_2 || Z_b = 68 || 56 || 359 \text{ k}\Omega = 28.3 \text{ k}\Omega$$

Output impedance \rightarrow

$$Z_o \approx R_c = 3.9 \text{ k}\Omega$$

Voltage gain \rightarrow

$$A_v = \frac{-h_{fe}(R_C || R_L)}{h_{ie} + R_E(1+h_{fe})} = \frac{-75 \times (3.9 \times 10^3 || 82 \times 10^3)}{2.1 \times 10^3 + 4.7 \times 10^3(1+75)} = -0.78$$

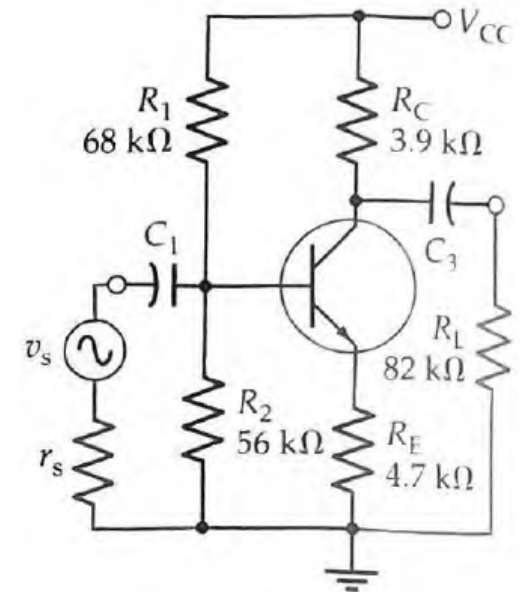

Common Collector Circuit Analysis

$$V_E = V_B - V_{BE}$$

ac signal is applied via C_1 to base
change in V_E is coupled via C_2 to load



Emitter follower →

input voltage = output voltage
no gain + no phase shift.

h -parameter equivalent circuit:

ac equivalent circuit →

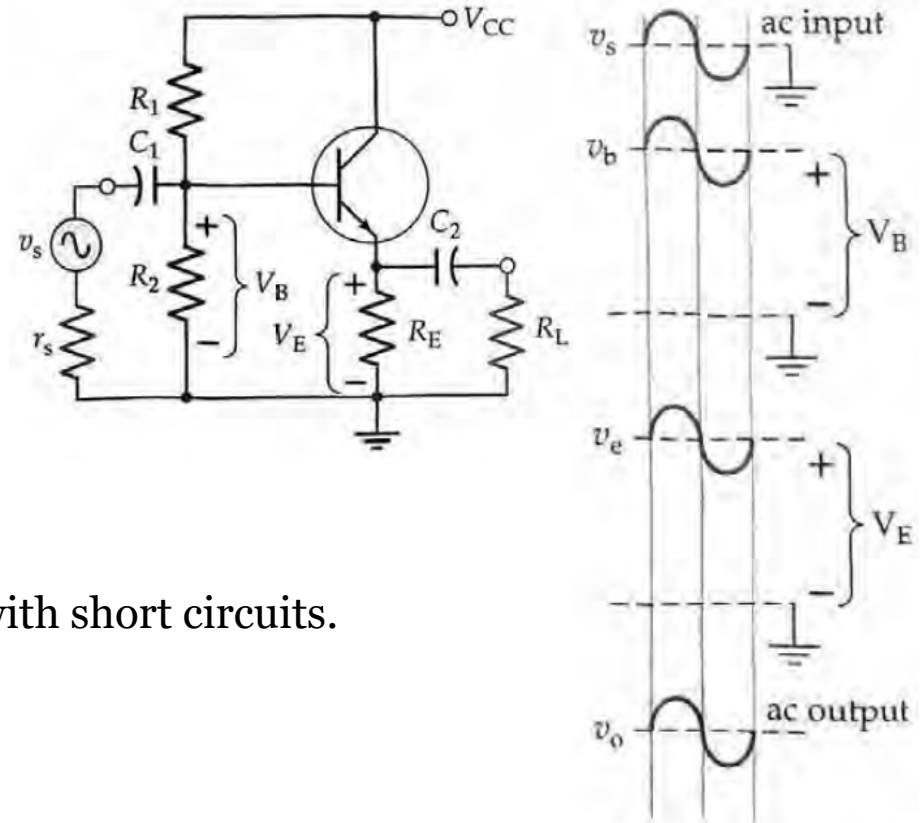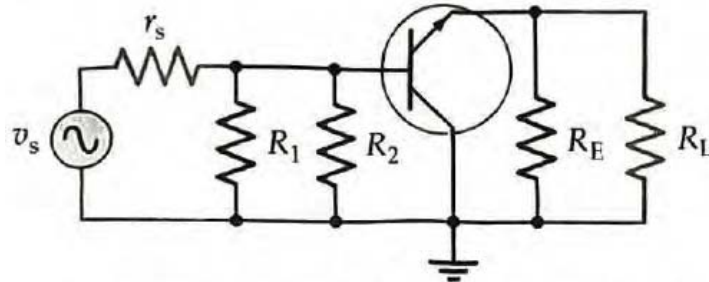
Power supply and capacitors are replaced with short circuits.





Common Collector Circuit Analysis

h -parameter equivalent circuit:

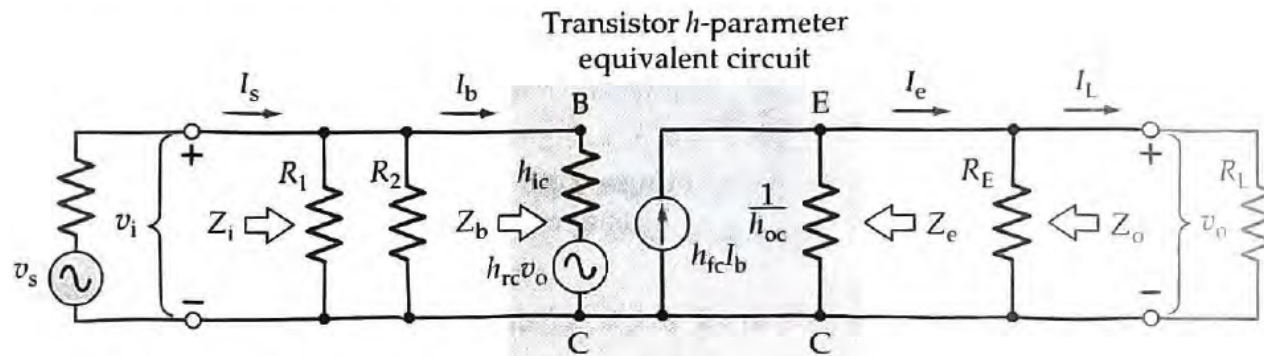Substitute transistor h -parameter model.



$h_{rc} = 1$
 v_o is fed back to input

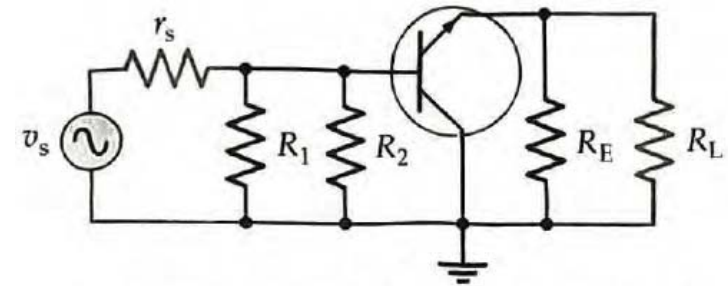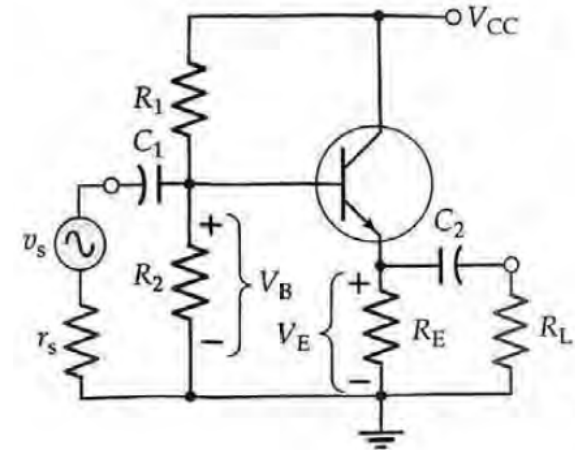

Common Collector Circuit Analysis

Input impedance:

$$Z_i = R_1 || R_2 || Z_b$$

$$Z_b = h_{ic} + h_{fc}(R_E || R_L)$$

Output impedance:

$$Z_o = Z_e || R_E$$

$$Z_e = \frac{h_{ic} + (R_1 || R_2 || r_s)}{h_{fc}}$$

Voltage gain:

$$v_i = I_b[h_{ic} + h_{fc}(R_E || R_L)]$$

$$v_o = I_e(R_E || R_L)$$

$$A_v = \frac{v_o}{v_i} = \frac{I_e(R_E || R_L)}{I_b[h_{ic} + h_{fc}(R_E || R_L)]} = \frac{(R_E || R_L)}{h_{ic} + (R_E || R_L)}$$

$$A_v \approx 1$$

