

EEE-2103: Electronic Devices and Circuits


Dept. of Computer Science and Engineering
University of Dhaka

Prof. Sazzad M.S. Imran, PhD
Dept. of Electrical and Electronic Engineering
sazzadmsi.webnode.com



Clippers

Simple parallel clippers:





NEGATIVE

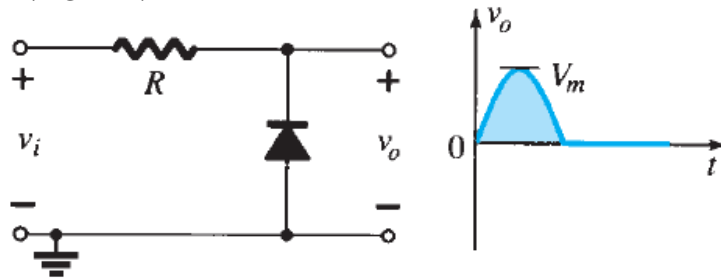

Biased series clippers:


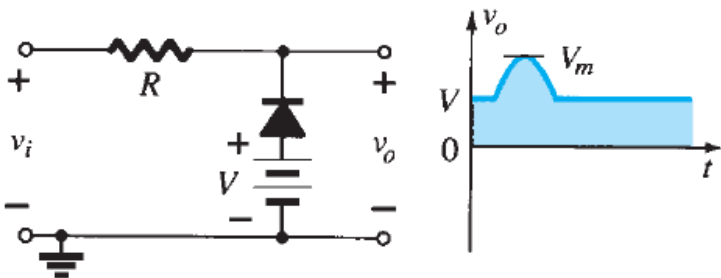
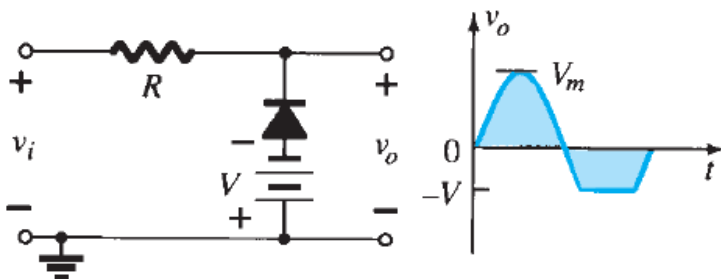


POSITIVE

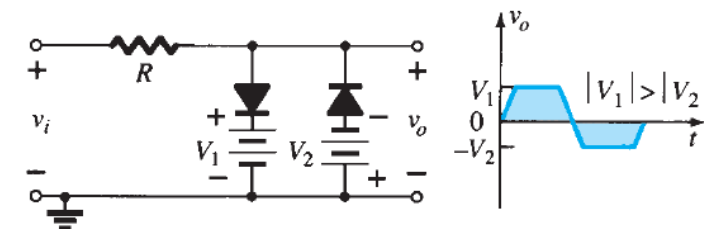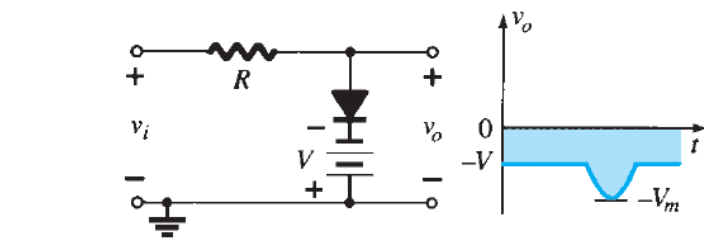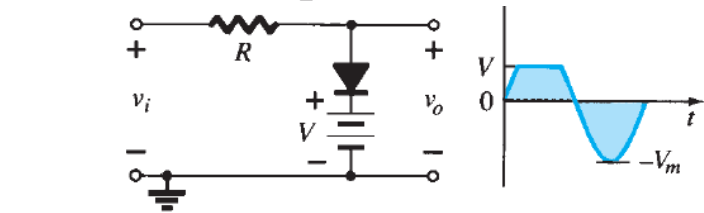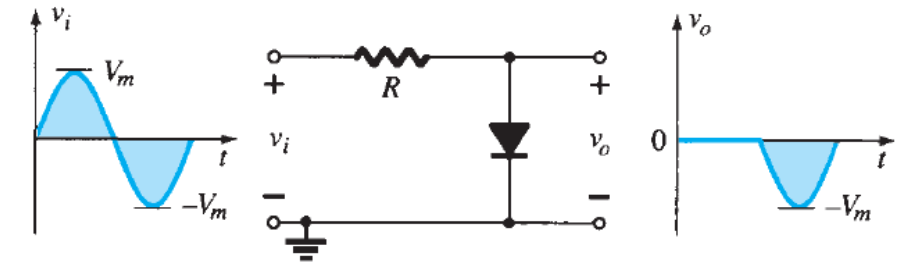


Clampers

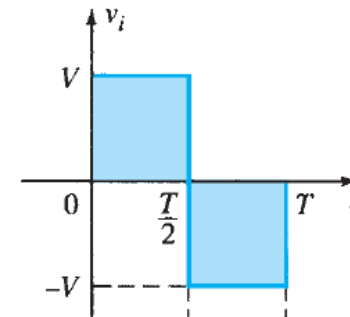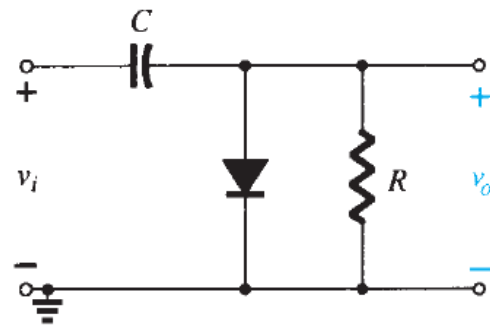
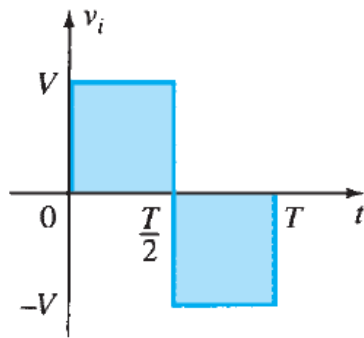
Clampers → shift applied signal to different dc level.
 don't change appearance of applied signal.
 constructed of diode, resistor, capacitor, dc supply.



For interval 0 to $T/2$

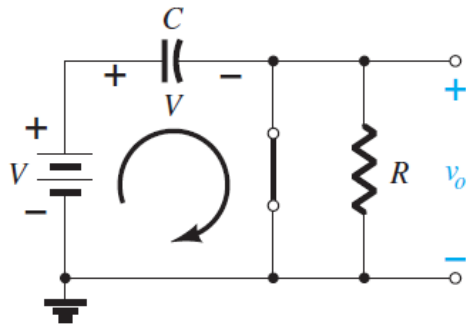



For period $T/2$ to T

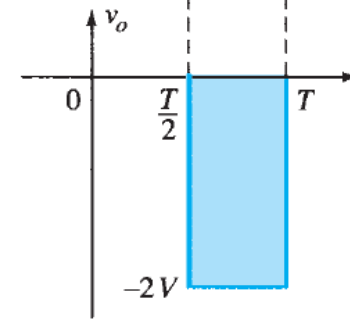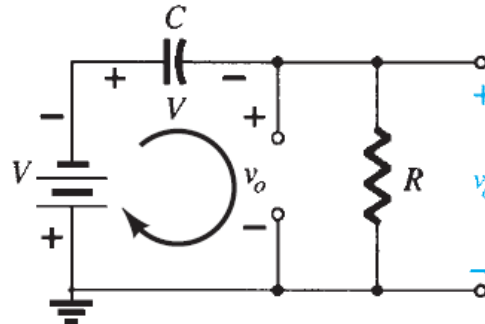

Clampers

Promble-19:

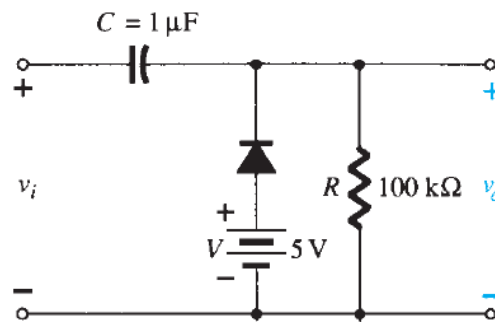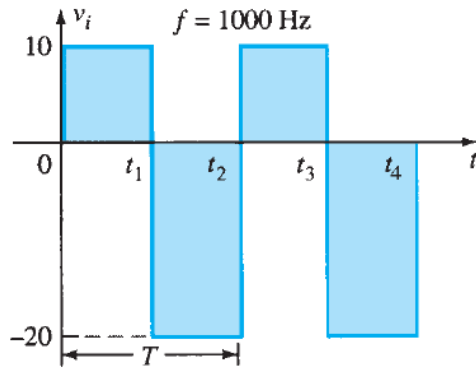Determine v_o for the network of Fig. 19 for the input indicated.



$$f_{in} = 1000 \text{ Hz}$$

$$T = 1/f = 1 \text{ ms, and interval between levels} = 0.5 \text{ ms.}$$

For period $t_1 \sim t_2 \rightarrow$


diode is in short-circuit state.

$$v_o = 5 \text{ V}$$

Applying Kirchhoff's voltage law




$$-20 \text{ V} + V_C - 5 \text{ V} = 0$$

$$V_C = 25 \text{ V}$$

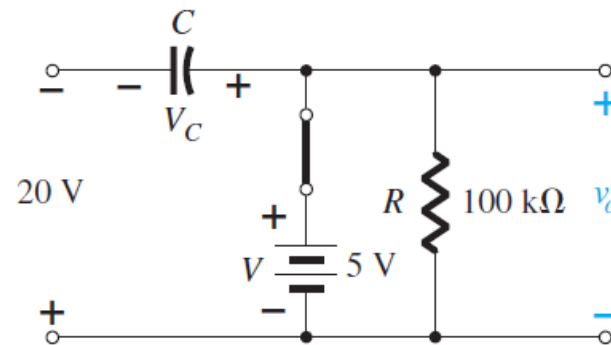


Clampers

Promble-19:

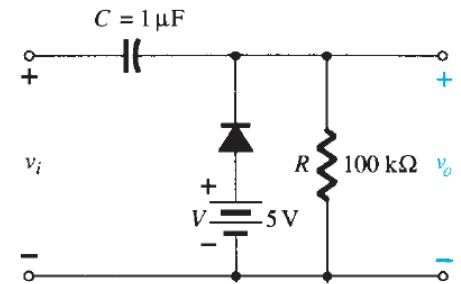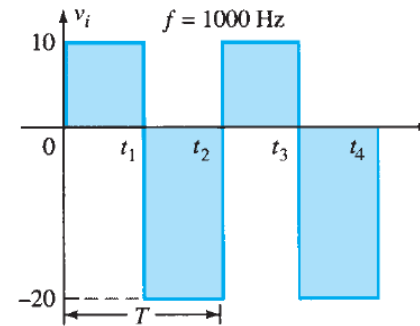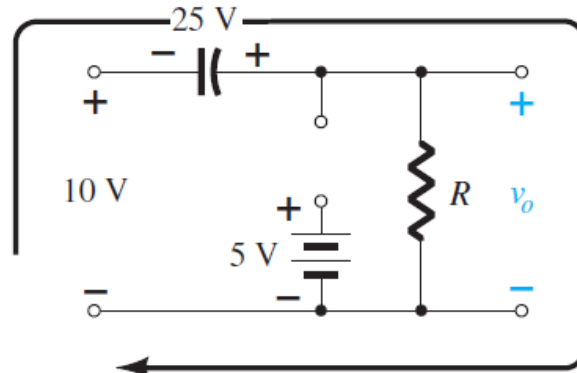

For period $t_2 \sim t_3 \rightarrow$ KVL
 diode is in open-circuit state.
 Applying Kirchhoff's voltage law
 $+10\text{ V} + 25\text{ V} - v_o = 0$
 $v_o = 35\text{ V}$



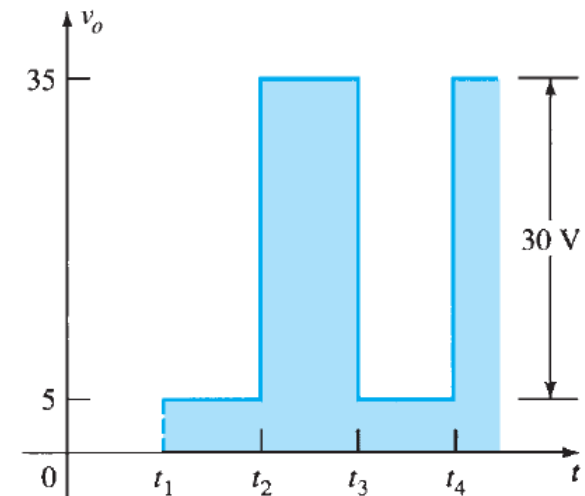
$\tau = RC = (100\text{ k}\Omega)(0.001\text{ mF}) = 0.1\text{ s} = 100\text{ ms}$
 total discharge time $= 5\tau = 5(100\text{ ms}) = 500\text{ ms}$.
 interval $t_2 \sim t_3 = 0.5\text{ ms}$
 capacitor will hold its voltage during discharge period.



Clampers

Promble-20:

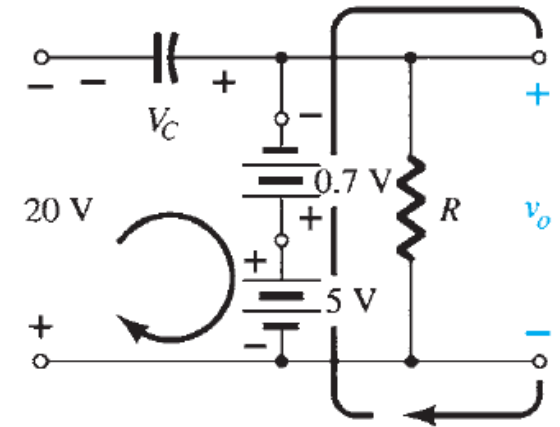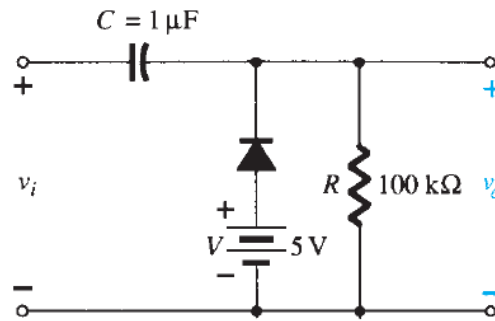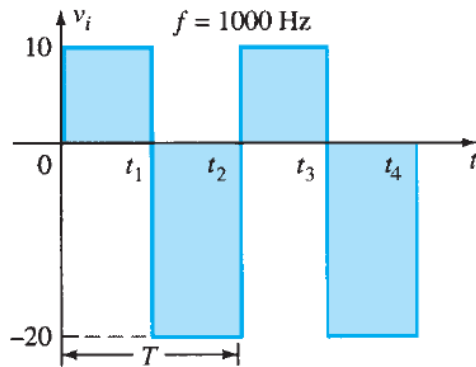Determine v_o for the network of Fig. 20 using a silicon diode with $V_K = 0.7$ V for the input indicated.



$f_{in} = 1000$ Hz
 $T = 1/f = 1$ ms, and interval between levels = 0.5 ms.

For period $t_1 \sim t_2 \rightarrow$

diode is in short-circuit state.

Applying Kirchhoff's voltage law

$$+5 \text{ V} - 0.7 \text{ V} - v_o = 0$$

$$v_o = 5 \text{ V} - 0.7 \text{ V} = 4.3 \text{ V}$$

Applying Kirchhoff's voltage law



$$-20 \text{ V} + V_C + 0.7 \text{ V} - 5 \text{ V} = 0$$

$$V_C = 25 \text{ V} - 0.7 \text{ V} = 24.3 \text{ V}$$



Clampers

Promble-20:

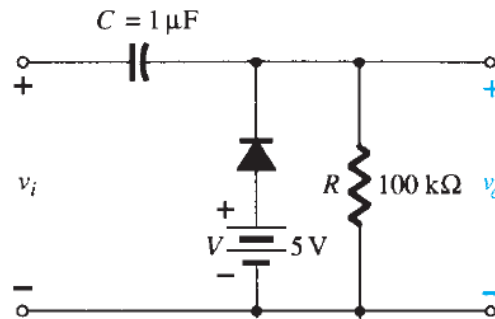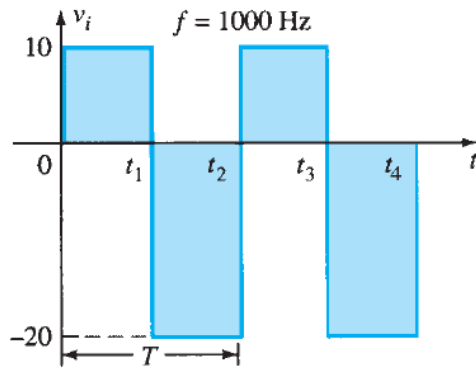Determine v_o for the network of Fig. 20 using a silicon diode with $V_K = 0.7 \text{ V}$ for the input indicated.



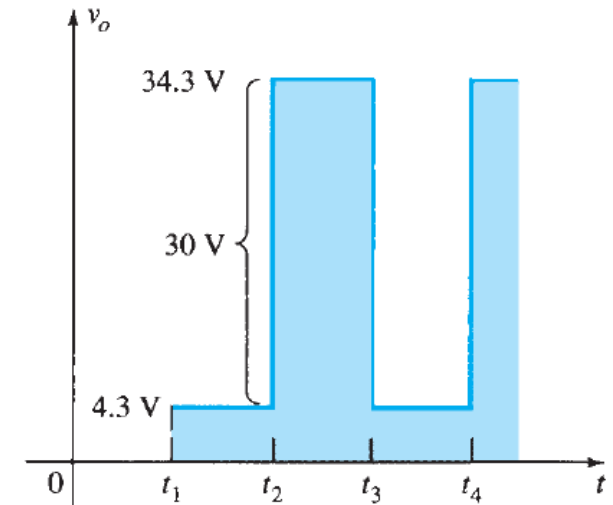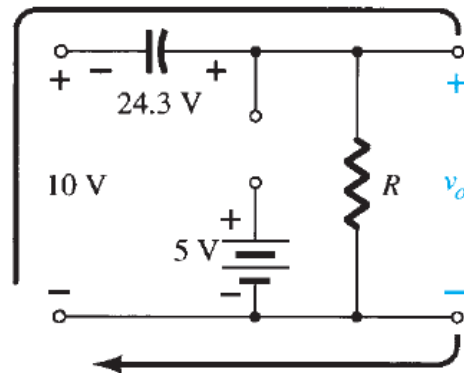For period $t_2 \sim t_3 \rightarrow$
 diode is in open-circuit state.
 Applying Kirchhoff's voltage law
 $+10 \text{ V} + 24.3 \text{ V} - v_o = 0$
 $v_o = 34.3 \text{ V}$



Clampers

Clamping networks:

