

EEE-2103: Electronic Devices and Circuits

Dept. of Computer Science and Engineering
University of Dhaka

Prof. Sazzad M.S. Imran, PhD
Dept. of Electrical and Electronic Engineering
sazzadmsi.webnode.com

Phase-Shift Oscillator

Feedback circuit = phase-shift oscillator.

Requirements for oscillation →

loop gain $\beta A > 1$

phase shift around feedback network is 180° .

Using classical network analysis →

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

$$\beta = \frac{1}{29} \rightarrow A > 29$$

Phase-shift = 180° .



Transistor phase-shift oscillator:

Resulting oscillator frequency:

$$f = \frac{1}{2\pi RC} \frac{1}{\sqrt{6+4(R_C/R)}}$$

To $\beta A > 1$, current gain of transistor:
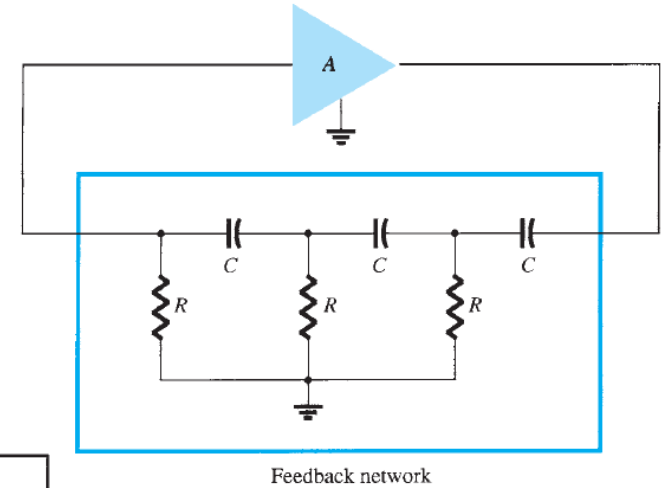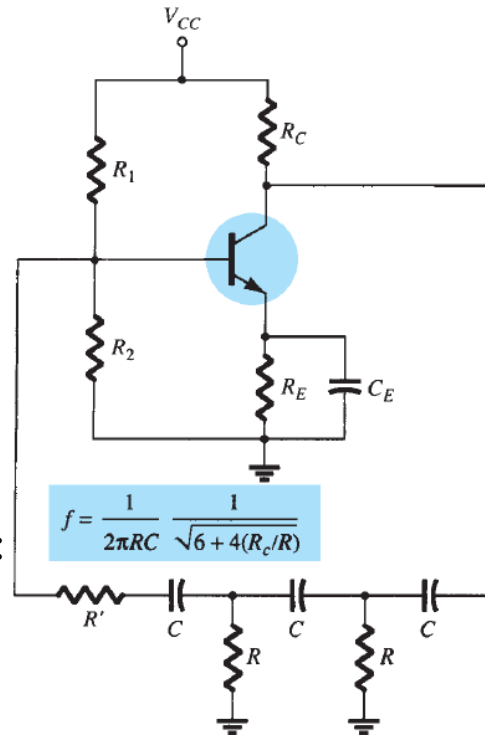
$$h_{fe} > 23 + 29 \frac{R}{R_C} + 4 \frac{R_C}{R}$$




Phase-Shift Oscillator

IC (op-amp) phase-shift oscillator:

Output of op-amp is fed to 3-stage RC network.

RC network provides $\rightarrow 180^\circ$ phase shift.
attenuation factor = $1/29$.

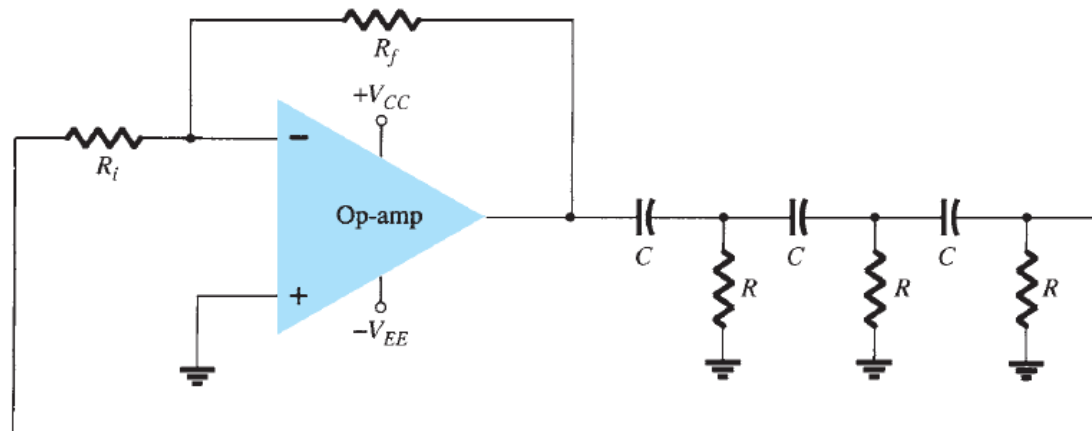Op-amp provides \rightarrow gain > 29 ($-R_f/R_i > 29$).



Wien Bridge Oscillator

IC (op-amp) phase-shift oscillator:

Oscillator circuit = op-amp + RC bridge circuit.

Oscillator frequency $\rightarrow R$ and C components.

R_1, R_2 and $C_1, C_2 \rightarrow$ frequency-adjustment elements,

R_3 and $R_4 \rightarrow$ part of feedback path.

Op-amp output \rightarrow points a and c .


Op-amp input \rightarrow points b and d .

Analysis of bridge circuit \rightarrow

$$\frac{R_3}{R_4} = \frac{R_1}{R_2} + \frac{C_2}{C_1} = 2 \quad [R_1 = R_2 = R]$$

$$[C_1 = C_2 = C]$$
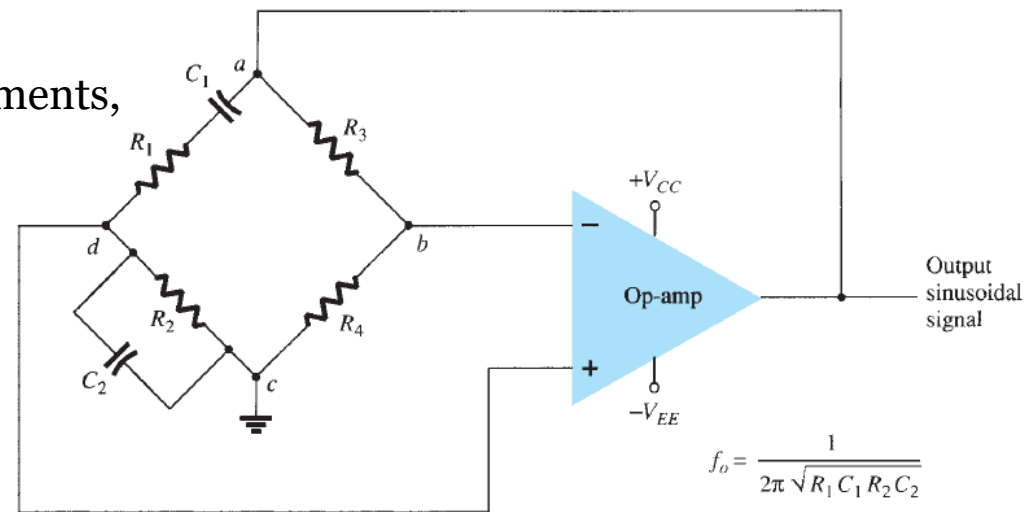
$$f_o = \frac{1}{2\pi\sqrt{R_1 C_1 R_2 C_2}} = \frac{1}{2\pi RC}$$



Wien Bridge Oscillator

Problem-50:


Calculate the resonant frequency of the Wien bridge oscillator of Fig. 50. Also, design the RC elements of a Wien bridge oscillator as in Fig. 50 for operation at $f_o = 10$ kHz.

$$f_o = \frac{1}{2\pi RC}$$
$$= \frac{1}{2\pi(51 \times 10^3)(0.001 \times 10^{-6})} = 3120.7 \text{ Hz}$$

Using equal values of R and C ,
select $R = 100 \text{ k}\Omega$

$$C = \frac{1}{2\pi f_o R} = \frac{1}{2\pi(10 \times 10^3)(100 \times 10^3)} = 159 \text{ pF}$$

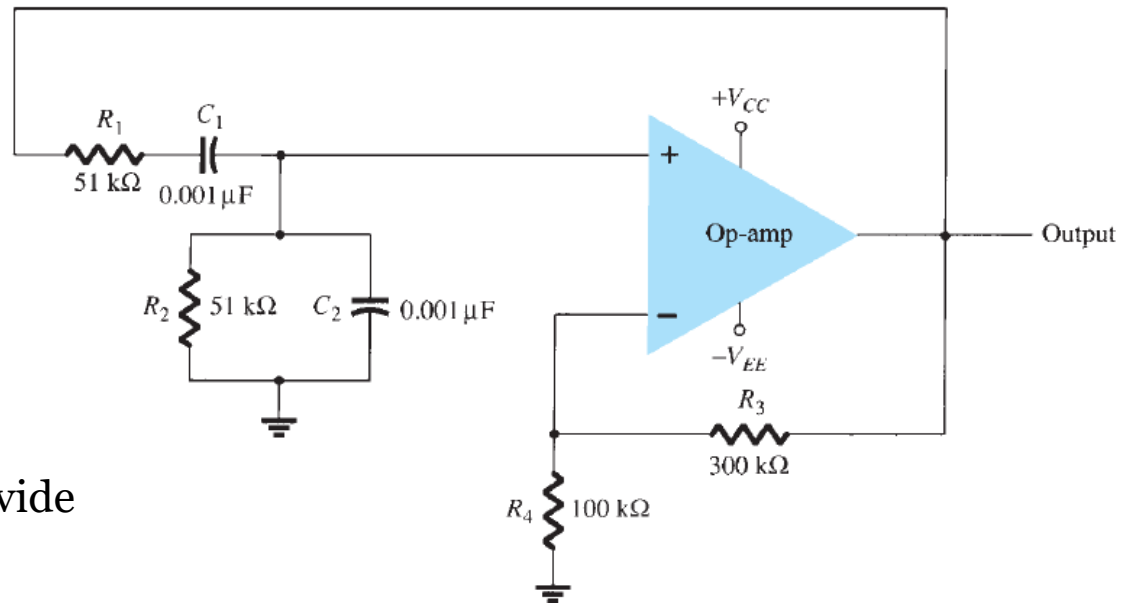
Let, $R_3 = 300 \text{ k}\Omega$ and $R_4 = 100 \text{ k}\Omega$ to provide
 $R_3/R_4 > 2$.



Tuned Oscillator

Tuned-input, tuned-output oscillator circuits →

<i>Oscillator Type</i>	<i>Reactance Element</i>		
	X_1	X_2	X_3
Colpitts oscillator	C	C	L
Hartley oscillator	L	L	C
Tuned input, tuned output	LC	LC	—

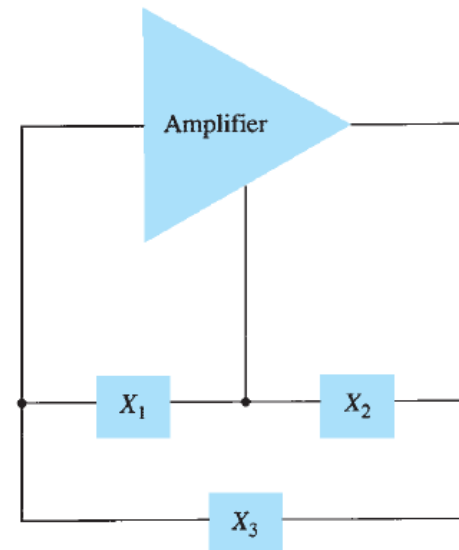

Tuned Oscillator

Colpitts oscillator →

CE amplifier + LC oscillator

feedback → voltage divider made of C_1 and C_2 in series across L .

Power supply is switched ON →

transistor starts to conduct, I_C increases.

C_1 and C_2 get charged to maximum →
start to discharge via L .


Electrostatic energy stored in C → magnetic flux.

Magnetic flux is stored within L as electromagnetic energy.

L starts to discharge, which charges C again.

Cycle continues → oscillations in tank circuit.

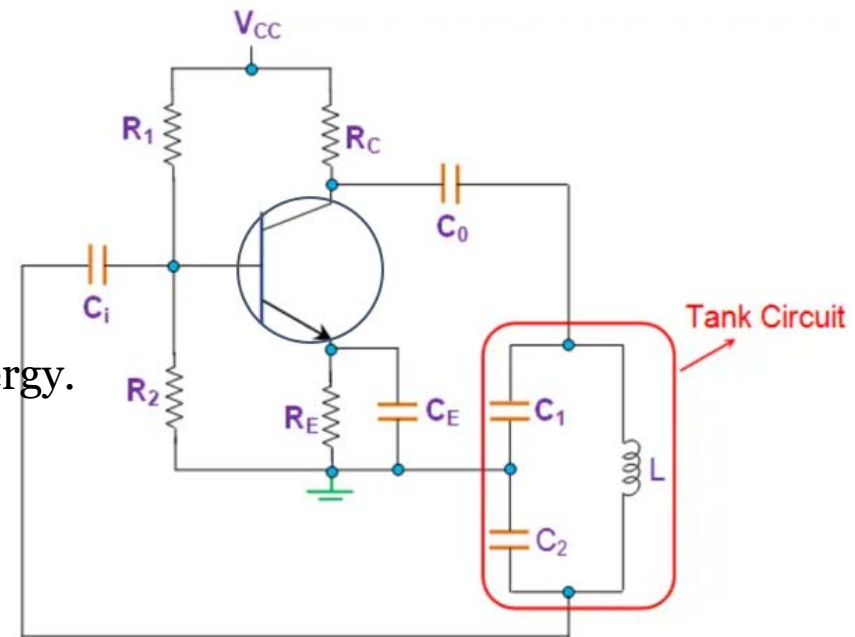V_{out} appears across C_1 and
in-phase with tank circuit's voltage →
makes-up for energy lost by re-supplying it.



Tuned Oscillator

Colpitts oscillator →

V_{fb} to transistor is obtained across C_2 ,
out-of-phase with voltage at transistor by 180° .

Point where C_1 and C_2 join is grounded →

V_{C1} and V_{C2} are opposite in polarity.

V_{fb} is provided with 180° phase-shift by transistor.


Net phase-shift around loop = 360° →

phase-shift criterion of Barkhausen principle.

Frequency of Colpitts oscillator depends on tank circuit.

$$f_o = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

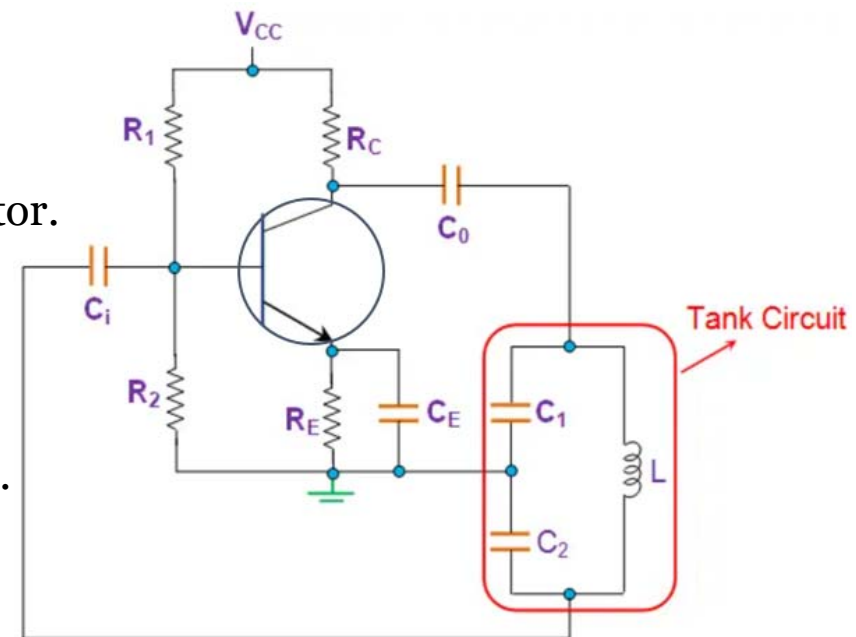

Tuned Oscillator

Hartley oscillator →

Gain = transistor amplifier.

Feedback = tuned LC circuit.

Phase change →

180° phase change V_B and V_C +

180° phase shift in feedback loop =


360° phase shift between V_{in} and V_{out} .

Frequency determining network →

parallel resonant circuit = L_1 and L_2 along with C .

L_1 and L_2 are inductively coupled.

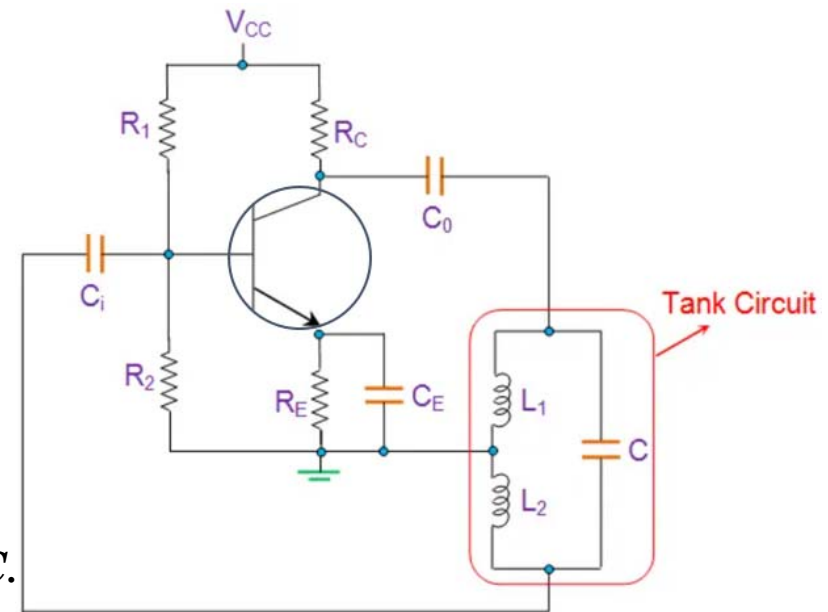L_1 is in output circuit and L_2 provides V_{fb} .



V_{CC} produces transient current in tank circuit → oscillatory current produces ac V_{L1} .

Frequency of Hartley oscillator depends on tank circuit.

$$f_o = \frac{1}{2\pi\sqrt{L_{eq}C}}, L_{eq} = L_1 + L_2$$

Integrated Circuits

Integrated circuit (IC) →

several components

interconnected in one small package

external connecting terminals →

input, output, supply voltage.

Classification (function) →

1) Analog – amplifiers, voltage regulators

2) Digital – logic gates, counting circuits

Classification (manufacturing) →

1) Monolithic

2) Hybrid

3) Thin film

4) Thick film

Integrated Circuits

Monolithic IC →

all components are fabricated on single chip of Si.
uses diffusion process – most economical for mass production.
interconnections are provided on surface of structure.
external connecting wires are taken out to terminals.

Thin film →

surface – glass or ceramic base.
depositing films of conducting material on surface.
resistors and conductors → different materials are selected
controls width and thickness of films.
capacitors → sandwiching film of insulating oxide
between two conducting films.
inductors → depositing metal film in spiral formation.
transistors and diodes → tiny discrete components are connected in circuit.

Integrated Circuits

Thick film →

printed thin-film circuits.

ceramic substrate – desired circuit pattern.

silk-screen printing techniques →

1) printing: conductive, resistive or dielectric pastes.

2) fuse films to substrate: circuits are fired at high temperature in furnace.

passive components – same way as thin film circuits.

active components – added as separate devices.

Hybrid or multichip IC→

interconnect number of individual chips.

active components – diffused transistors or diodes.

passive components – group of diffused resistors or capacitors on single chip.
thin film components.

connections between chips – fine wire or metal film.

expensive for mass production; economical for small quantities.

better performance than monolithic circuits.