

# **EEE-2103: Electronic Devices and Circuits**

Dept. of Computer Science and Engineering  
University of Dhaka

Prof. Sazzad M.S. Imran, PhD  
Dept. of Electrical and Electronic Engineering  
[sazzadmsi.webnode.com](http://sazzadmsi.webnode.com)

# Common-Base Configuration

## Alpha ( $\alpha$ )

Current gain in CB configuration.



$$\alpha = I_C / I_E$$

$$\approx 1 = 0.9 \sim 0.998$$

$I_C$  and  $I_E$  = levels of current at point of operation

$\alpha$  is defined solely for majority carriers  $\rightarrow$

$$I_C = \alpha I_E + I_{CBO}$$

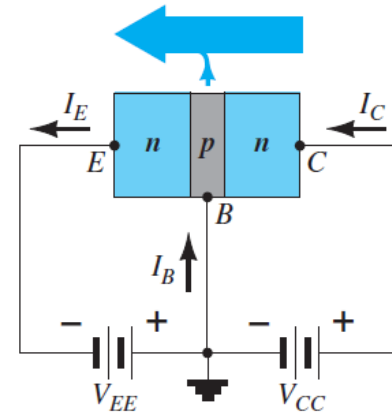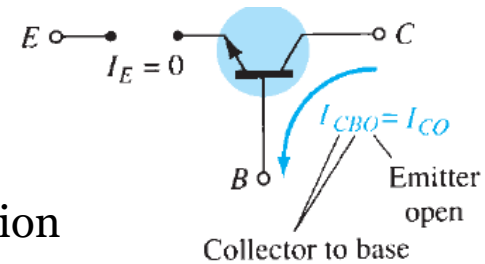

# Common-Emitter Configuration

Most frequently encountered configuration

CE configuration →

emitter is common to both input and output  
common to both base and collector

Two sets of characteristics →


one for input or base-emitter circuit

one for output or collector-emitter circuit.

Current relations for common-base configuration  
are applicable →

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

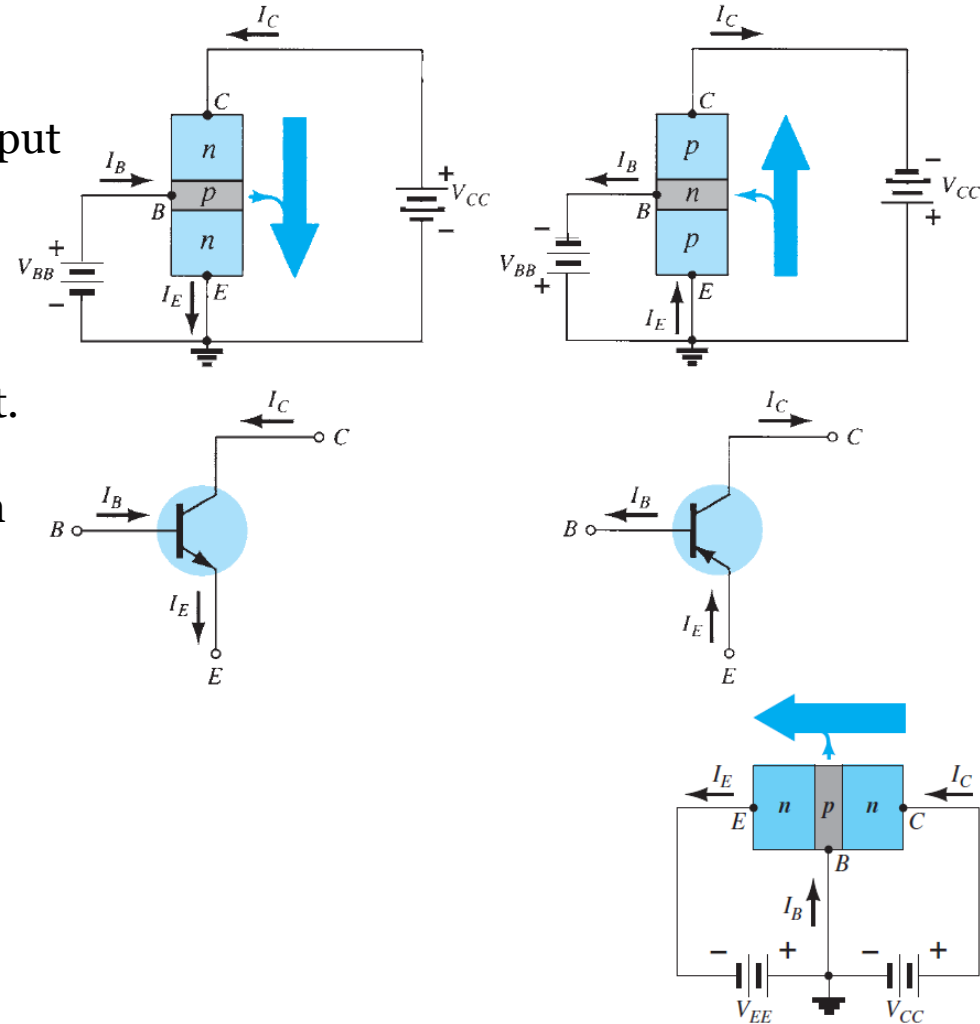



# Common-Emitter Configuration

Input characteristics →

input current ( $I_B$ ) versus input voltage ( $V_{BE}$ )  
range of values of output voltage ( $V_{CE}$ ).

Output characteristics →

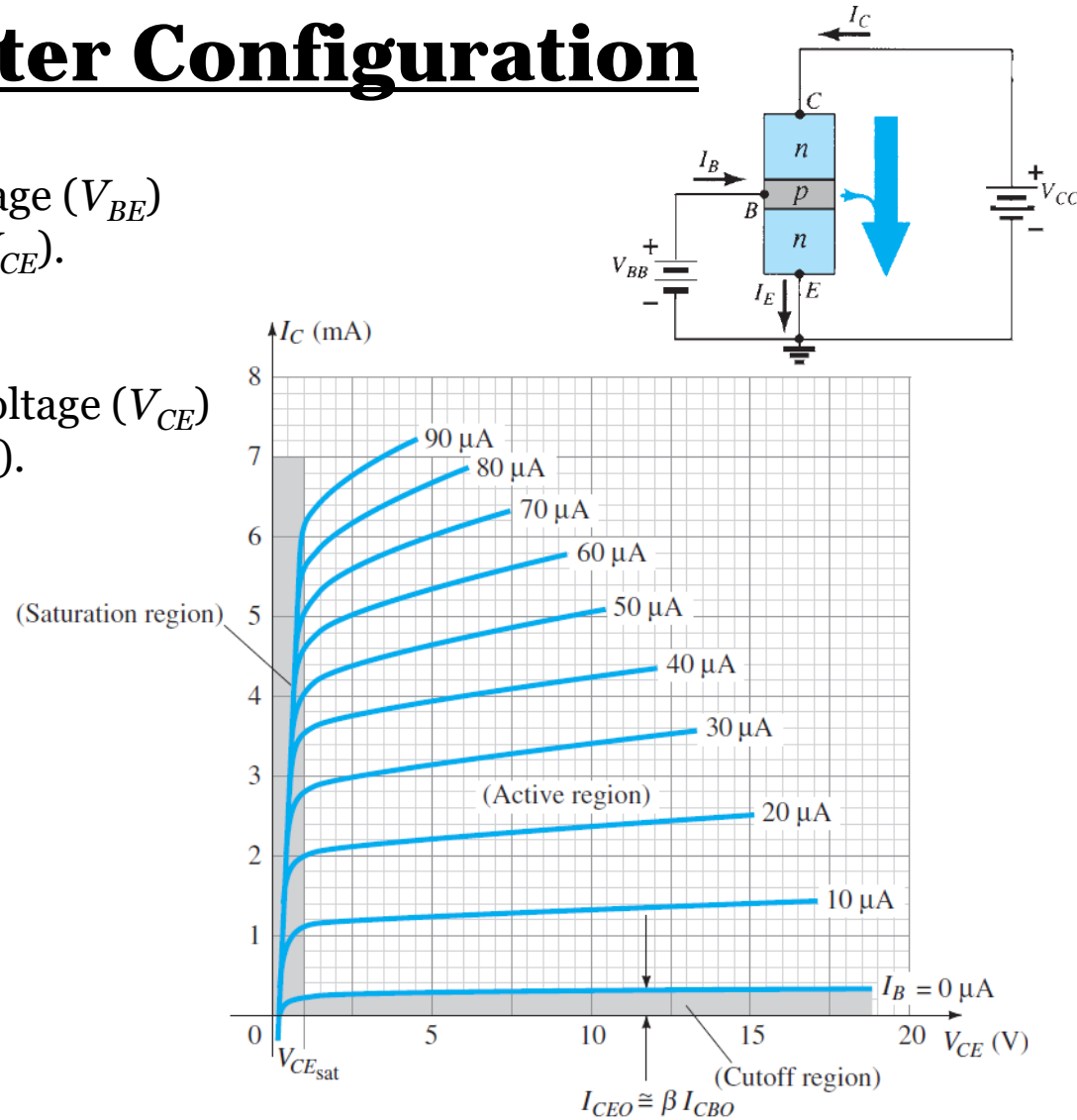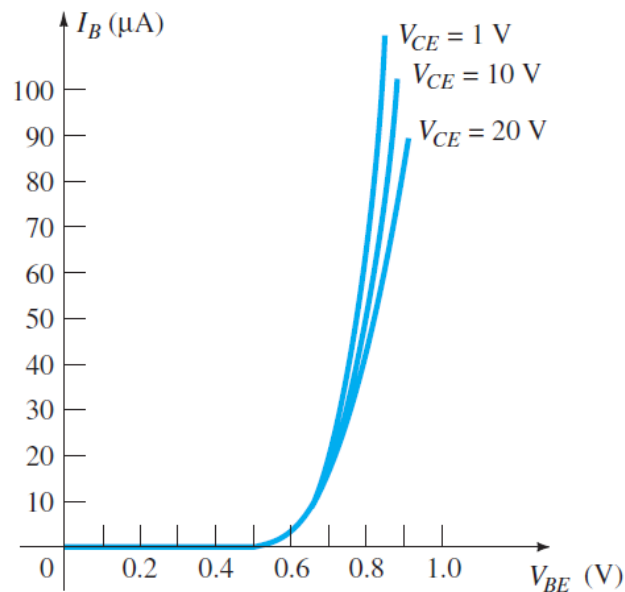output current ( $I_C$ ) versus output voltage ( $V_{CE}$ )  
range of values of input current ( $I_B$ ).



# Common-Emitter Configuration

Output characteristics →

$V_{CE}$  influences  $I_C$

Active region →

region in which curves for  $I_B$  are nearly straight and equally spaced.

base-emitter junction is forward-biased,  
collector-base junction is reverse-biased.



voltage, current, or power amplification.

Cutoff region →

$I_C \neq 0$  when  $I_B = 0$ .

CB configuration →

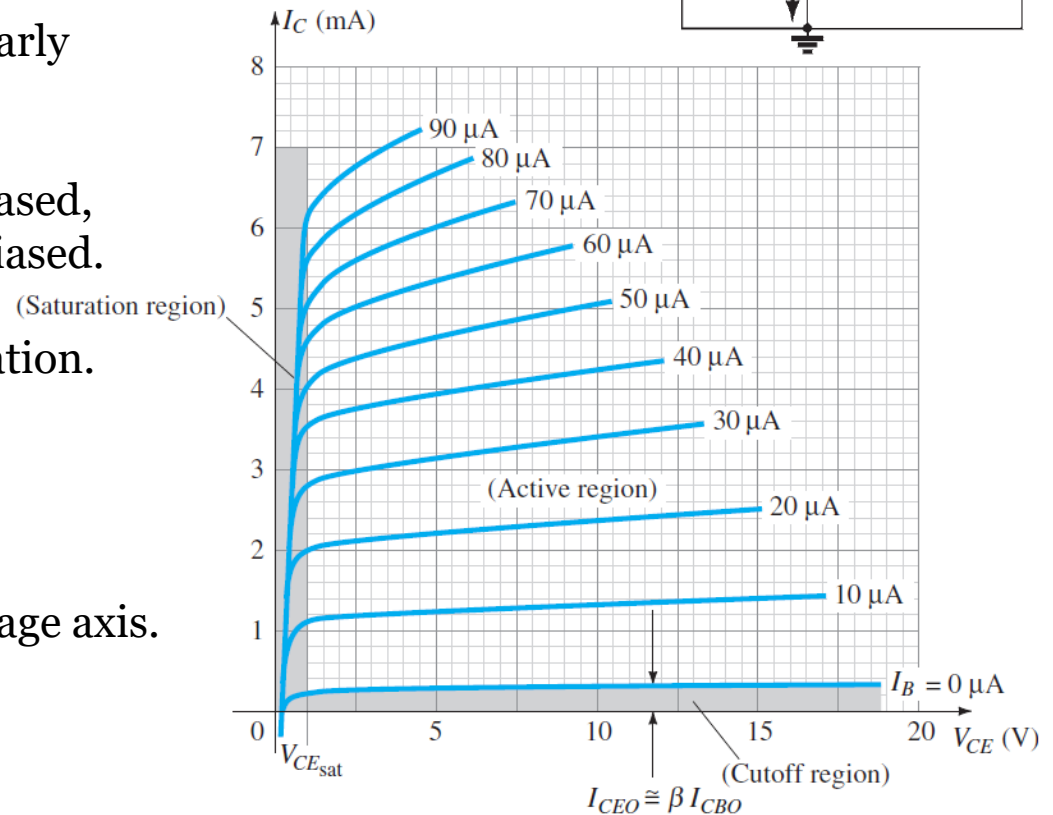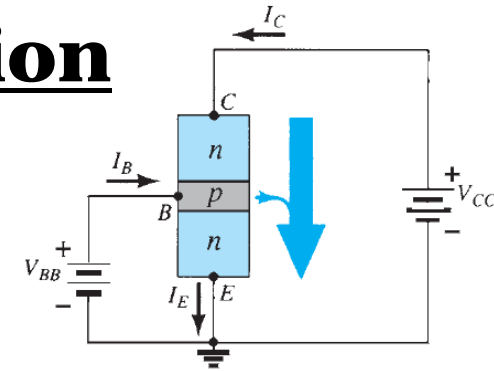$I_E = 0$ ,  $I_C = I_{CO}$ , curve  $I_E = 0 \Rightarrow$  voltage axis.



# Common-Emitter Configuration

Cutoff region →

$$I_C = \alpha I_E + I_{CBO} = \alpha(I_C + I_B) + I_{CBO}$$

$$I_C = \frac{\alpha I_B}{1-\alpha} + \frac{I_{CBO}}{1-\alpha}$$

$$I_B = 0 \text{ and } \alpha = 0.996$$




$$I_C = \frac{\alpha(0)}{1-\alpha} + \frac{I_{CBO}}{1-0.996} = 250 I_{CBO}$$

$$I_C = I_{CEO} = \frac{I_{CBO}}{1-\alpha} \Big|_{I_B=0 \mu A}$$

$$\text{If } I_{CBO} = 1 \mu A, I_B = 0 A \rightarrow$$

$$I_C = 250(1 \mu A) = 0.25 \text{ mA}$$

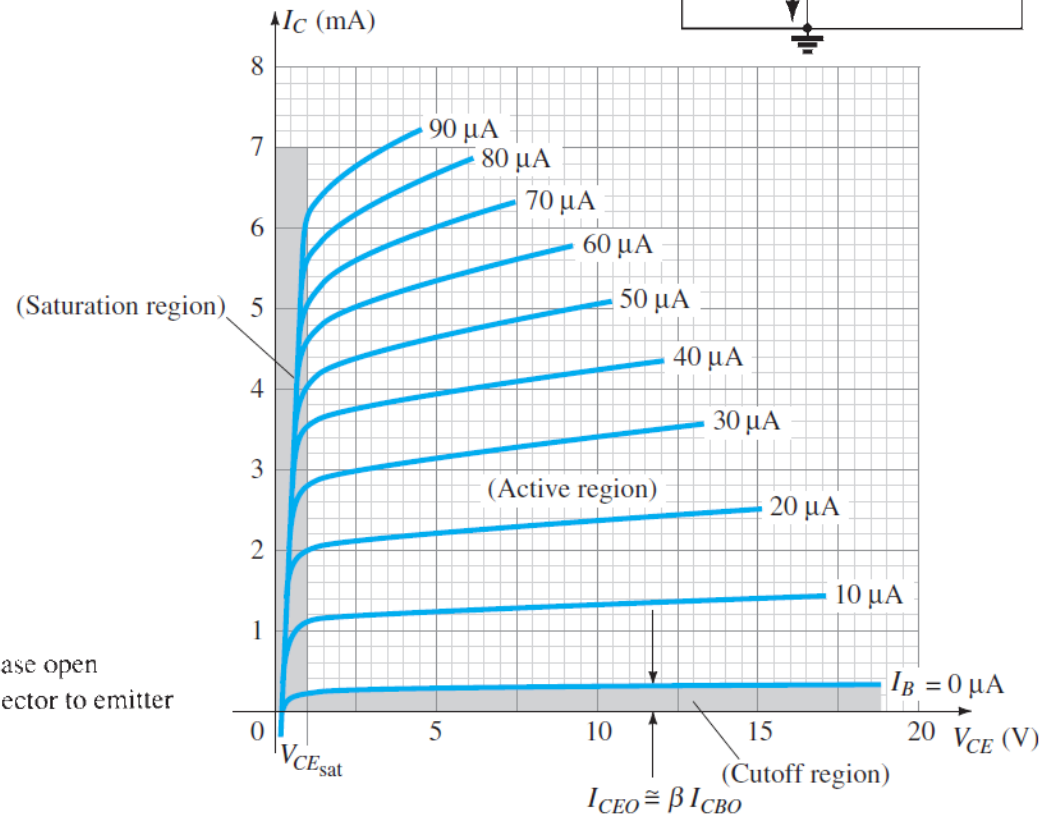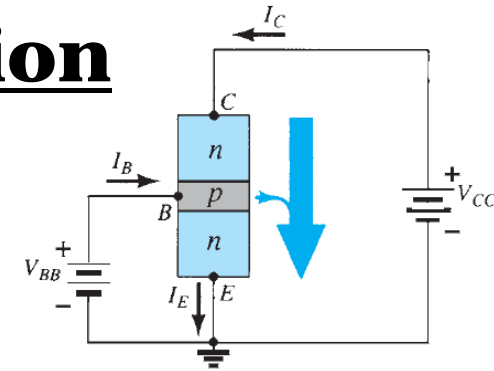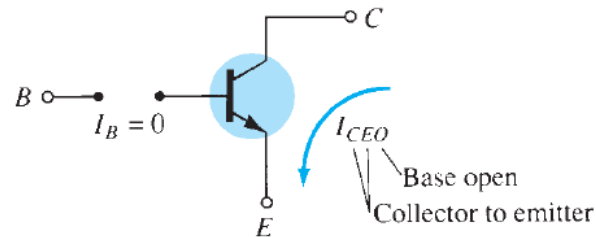region below  $I_B = 0 \text{ mA}$  is to be avoided if undistorted output signal is required.



# Common-Emitter Configuration

Beta ( $\beta$ ):

Common-emitter, forward-current, amplification factor.

$$\beta = I_C/I_B \approx 50 \text{ to over } 400$$

referred to as  $h_{FE}$

[ $h$  = hybrid equivalent circuit]

Relationship between  $\beta$  and  $\alpha$ :

$$\beta = I_C/I_B \rightarrow I_B = I_C/\beta$$

$$\alpha = I_C/I_E \rightarrow I_E = I_C/\alpha$$

$$I_E = I_C + I_B$$


$$I_C/\alpha = I_C + I_C/\beta \rightarrow 1/\alpha = 1 + 1/\beta$$

$$\rightarrow \beta = \alpha\beta + \alpha = \alpha(\beta+1)$$

$$\alpha = \frac{\beta}{\beta+1} \text{ and } \beta = \frac{\alpha}{1-\alpha}$$





$$I_C = \beta I_B$$
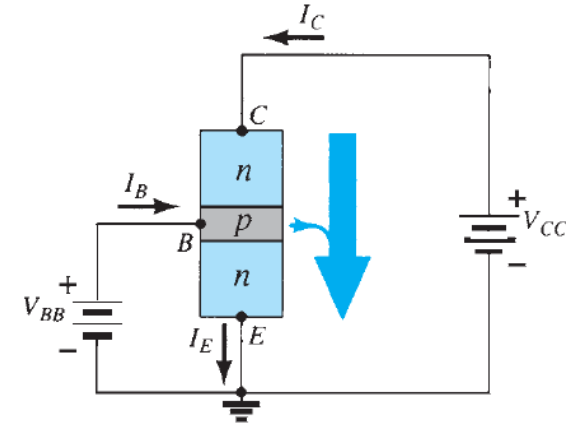
$$I_E = I_C + I_B = \beta I_B + I_B = (\beta + 1)I_B$$



# Common-Emitter Configuration

Biassing in active region:

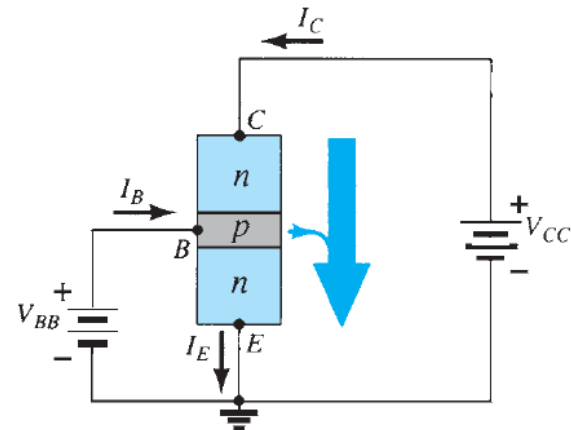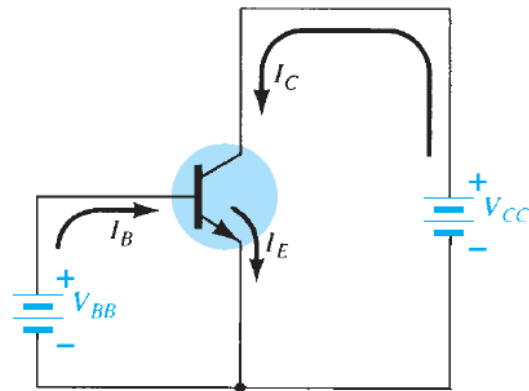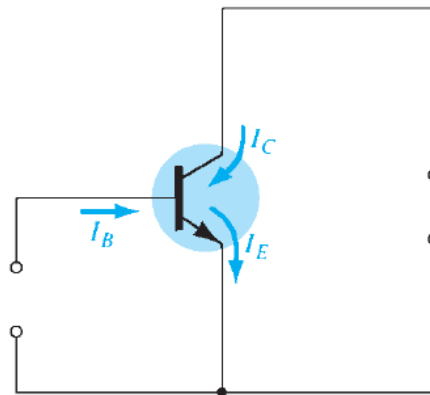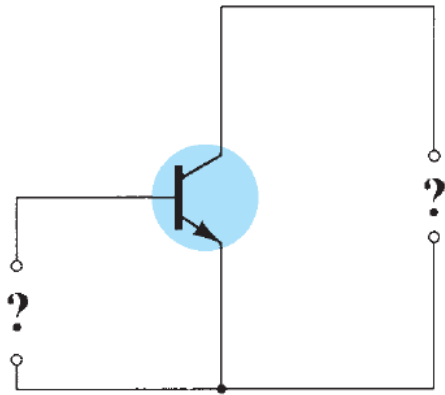



# Common-Collector Configuration



Used for impedance-matching purposes.  
High input impedance and low output impedance.

Input characteristics →

$I_B$  decreases as  $V_{BC}$  is increased

Drop in  $I_B$  is delayed if  $V_{EC}$  is increased

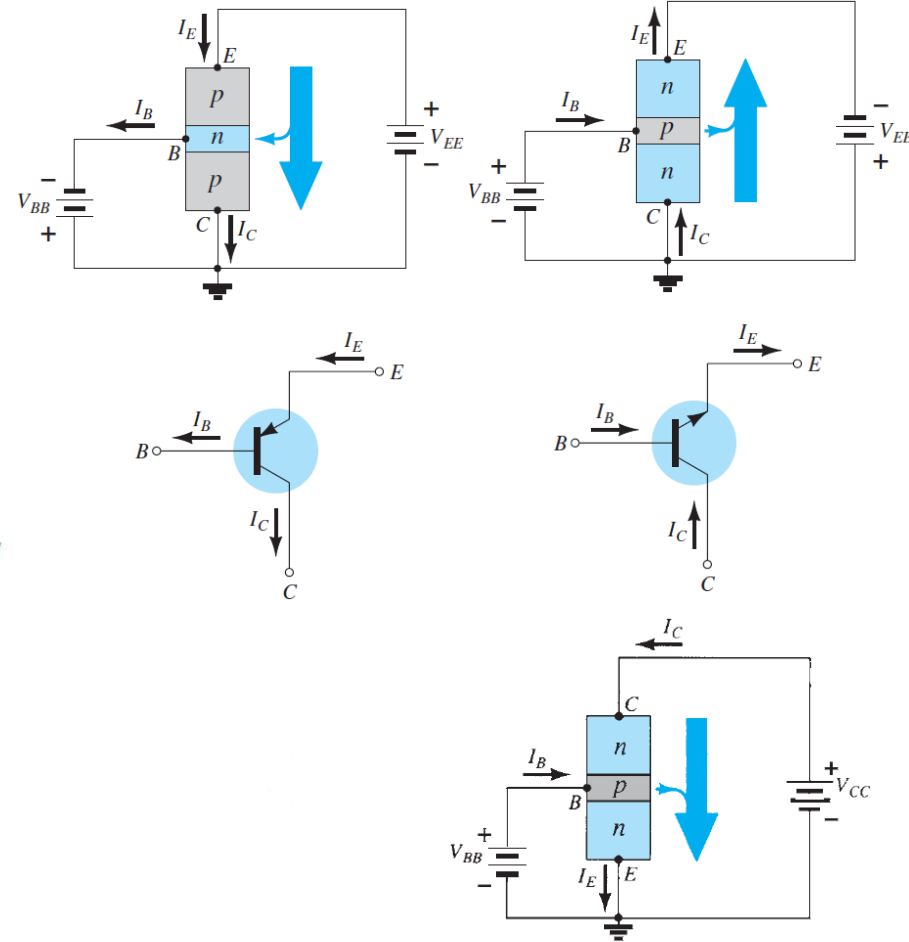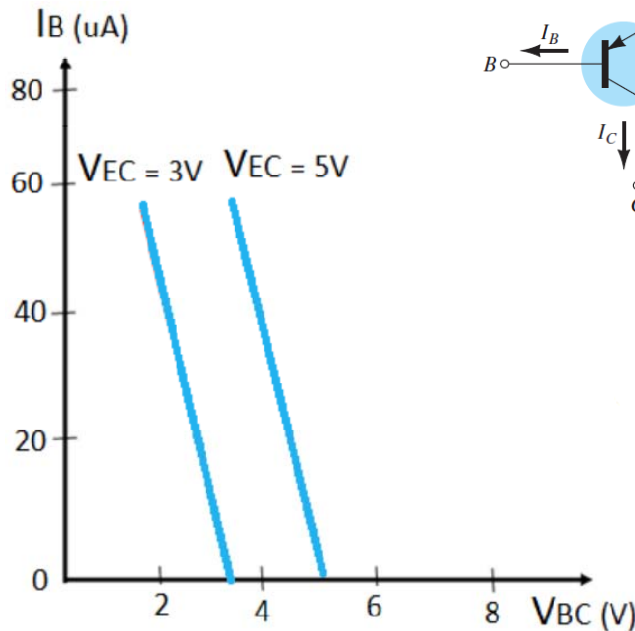$V_{EC} = V_{EB} + V_{BC} \rightarrow V_{EB} = V_{EC} - V_{BC}$   
Increasing  $V_{BC}$  with  $V_{EC} = \text{const.}$   
Reduces  $V_{EB} \rightarrow$  reduces  $I_B$



# Common-Collector Configuration

Output characteristics of CC configuration =  
Output characteristics for CE configuration.

Output characteristics  $\rightarrow$  plot of  $I_E$  versus  $V_{CE}$   
range of values of  $I_B$ .  
 $I_C = \alpha I_E \rightarrow I_C \approx I_E [\alpha \approx 1]$

