

EEE-2103: Electronic Devices and Circuits

Dept. of Computer Science and Engineering
University of Dhaka

Prof. Sazzad M.S. Imran, PhD
Dept. of Electrical and Electronic Engineering
sazzadmsi.webnode.com

Transistor Construction

Transistor →

three-layer semiconductor device

pnp = two *p* - and one *n* -type layers

npn = two *n* - and one *p* -type layers

E = emitter, *C* = collector, *B* = base





emitter layer is heavily doped,
base and collector are lightly doped

total width : center layer = 150:1

sandwiched layer doping : outer layers doping $\leq 1:10$

BJT = bipolar junction transistor

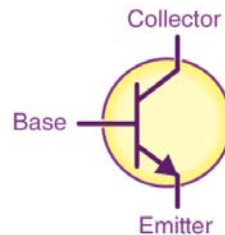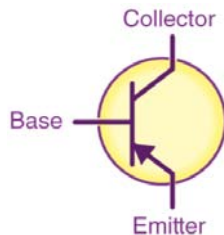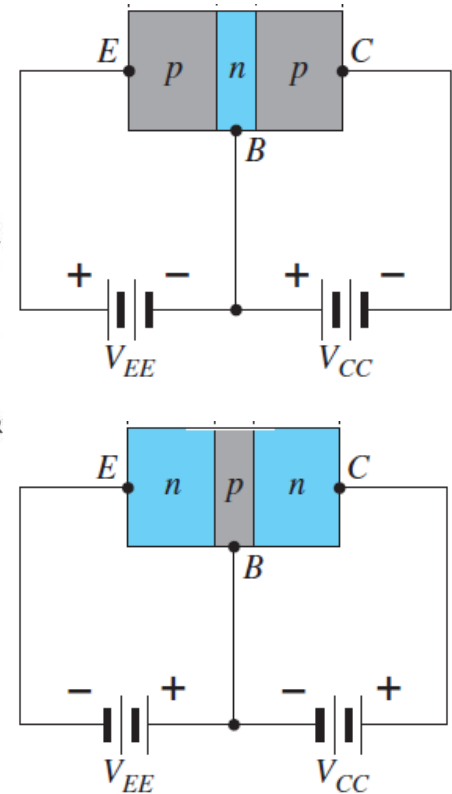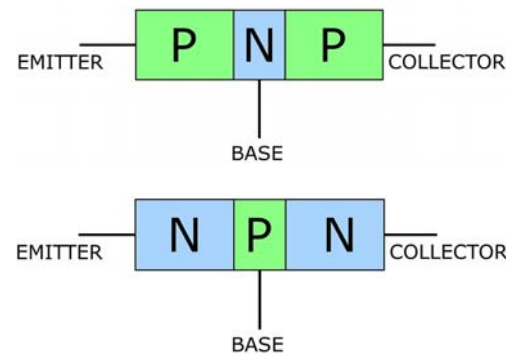bipolar = both holes and electrons participate in injection process



Transistor Operation


One p - n junction is reverse-biased
Another p - n junction is forward-biased.

Large number of majority carriers diffuse across forward biased p - n junction into n -type material.

Sandwiched n -type material is very thin and has low conductivity.
very small number of majority carriers \rightarrow base terminal.

For reverse-biased junction \rightarrow
injected majority carriers = minority carriers in n -type base region.
Larger number of majority carriers +
all minority carriers in depletion region \rightarrow
diffuse across reverse-biased junction into p -type.

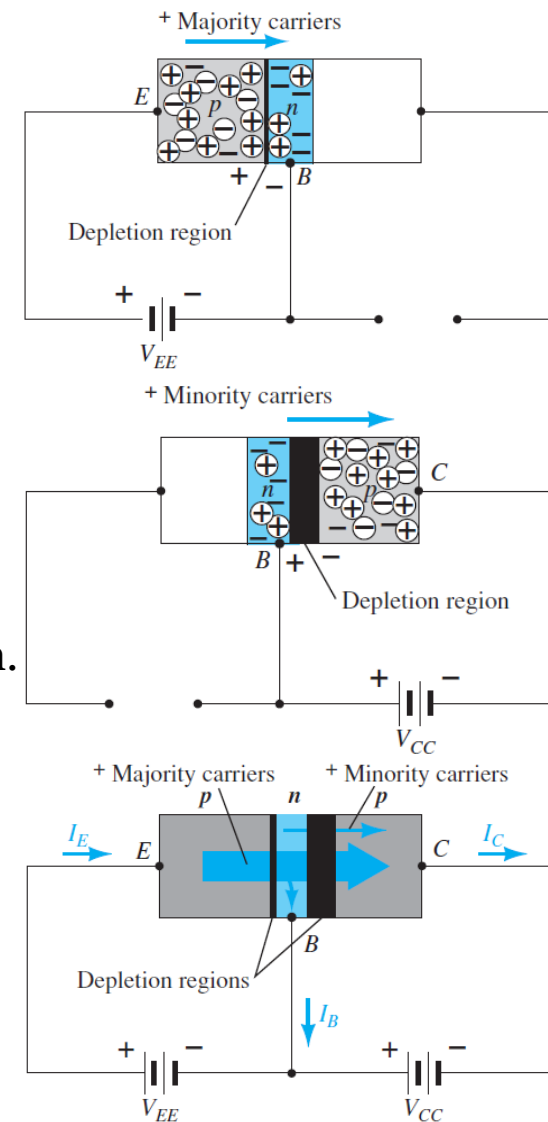$I_B \approx$ microamperes,
 $I_E \approx$ milliamperes.



Transistor Operation

Applying Kirchhoff's current law

$$I_E = I_C + I_B$$

Collector current = majority + minority carriers

Minority-current component = I_{CO} = leakage current

$I_{CO} = I_C$ current with emitter terminal Open


$$I_C = I_{C\text{majority}} + I_{CO\text{minority}}$$

$I_C \approx$ milliamperes

$I_{CO} \approx$ microamperes or nanoamperes

$I_B \approx$ microamperes,

$I_E \approx$ milliamperes.

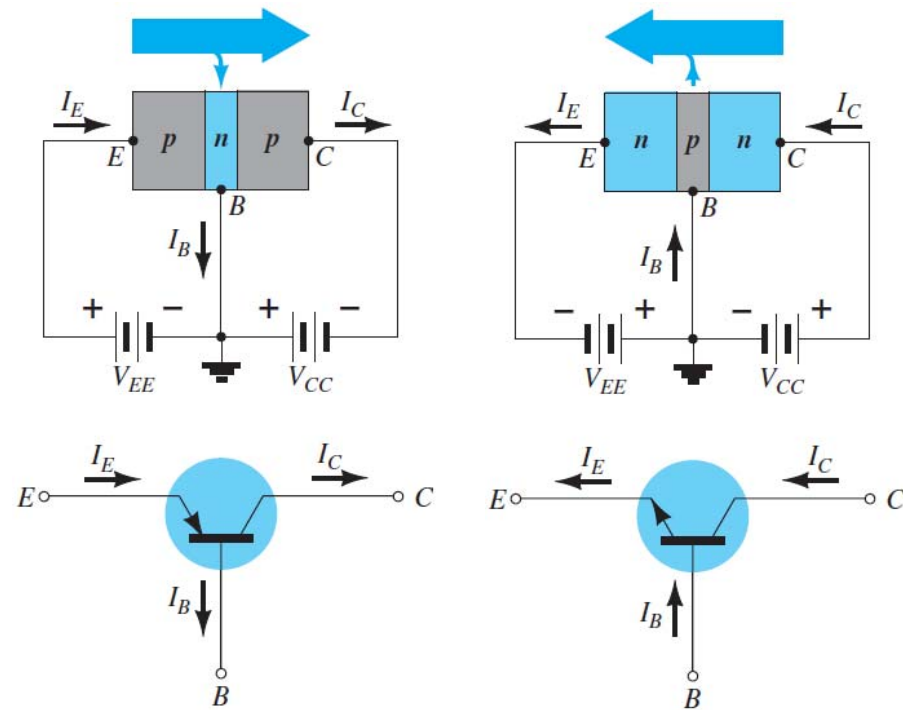

Common-Base Configuration

Common-base terminology →

base is common to both input and output
base is closest to, or at, ground potential.

$$I_E = I_C + I_B$$


biasing voltage sources establish current such that

$V_{EE} \rightarrow$ direction of I_E

$V_{CC} \rightarrow$ direction of I_C

Two sets of characteristics →

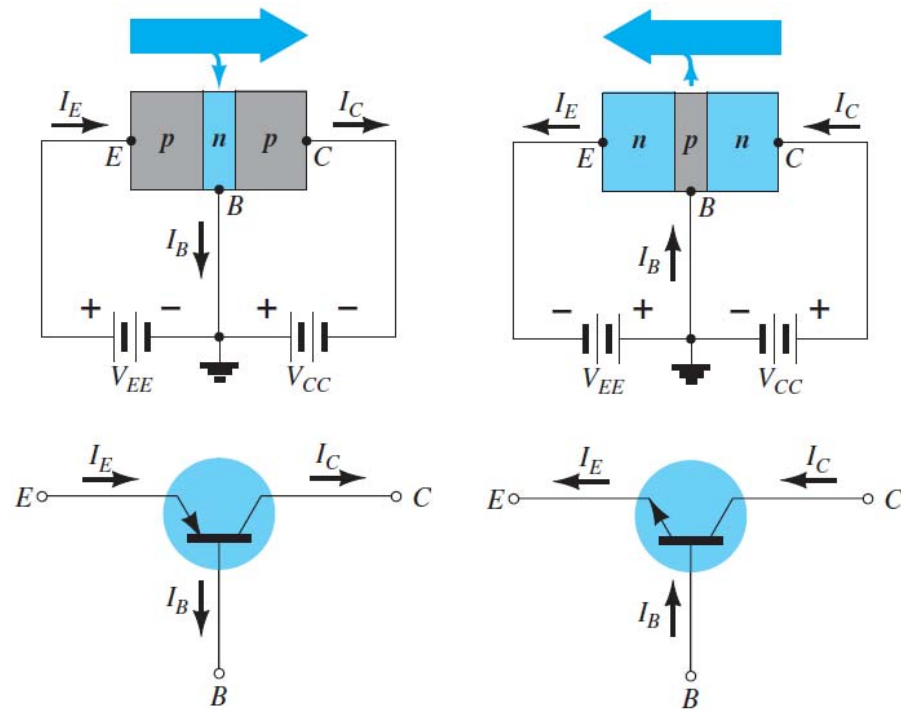- i) driving point or input parameters
- ii) output side.





Common-Base Configuration

Input set for CB configuration →

input current (I_E) to input voltage (V_{BE})

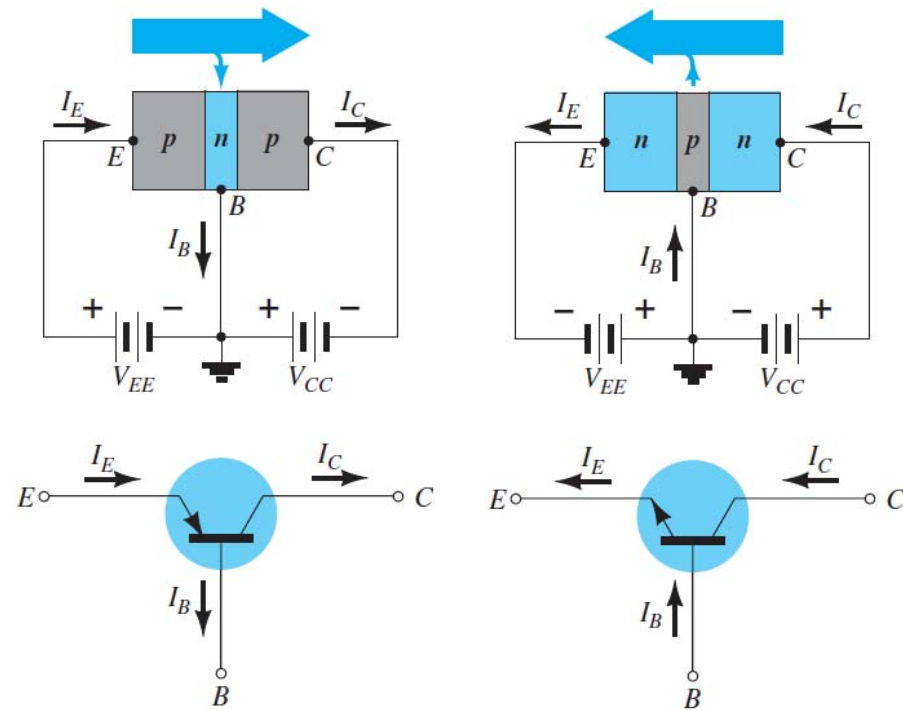
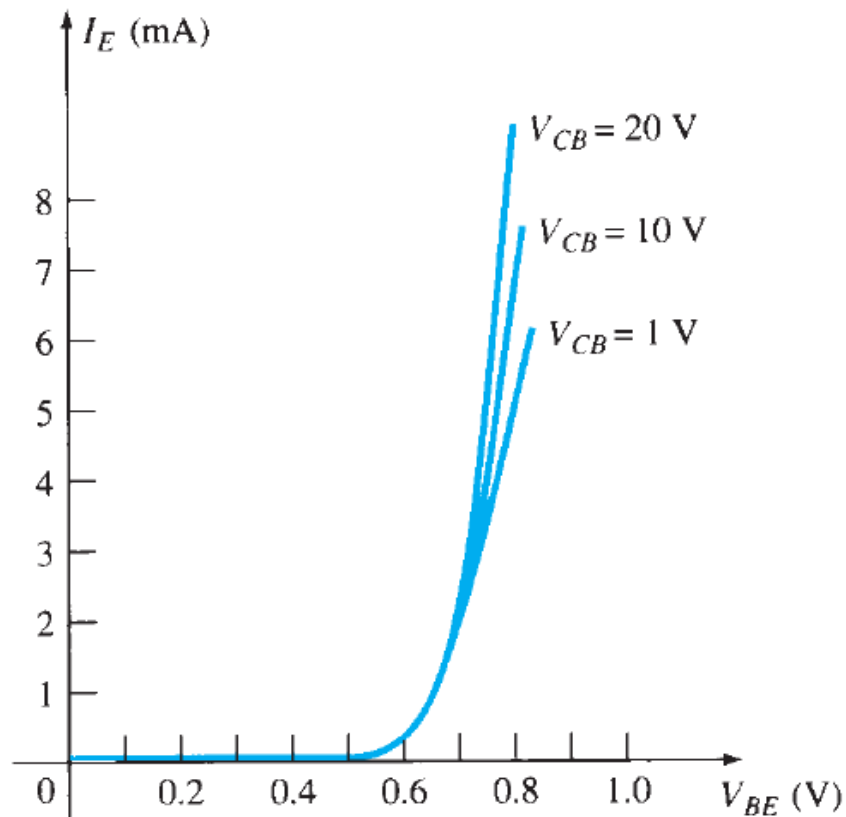
various levels of output voltage (V_{CB})



Common-Base Configuration

Output set for CB configuration →
output current (I_C) to output voltage (V_{CB})
various levels of input current (I_E)

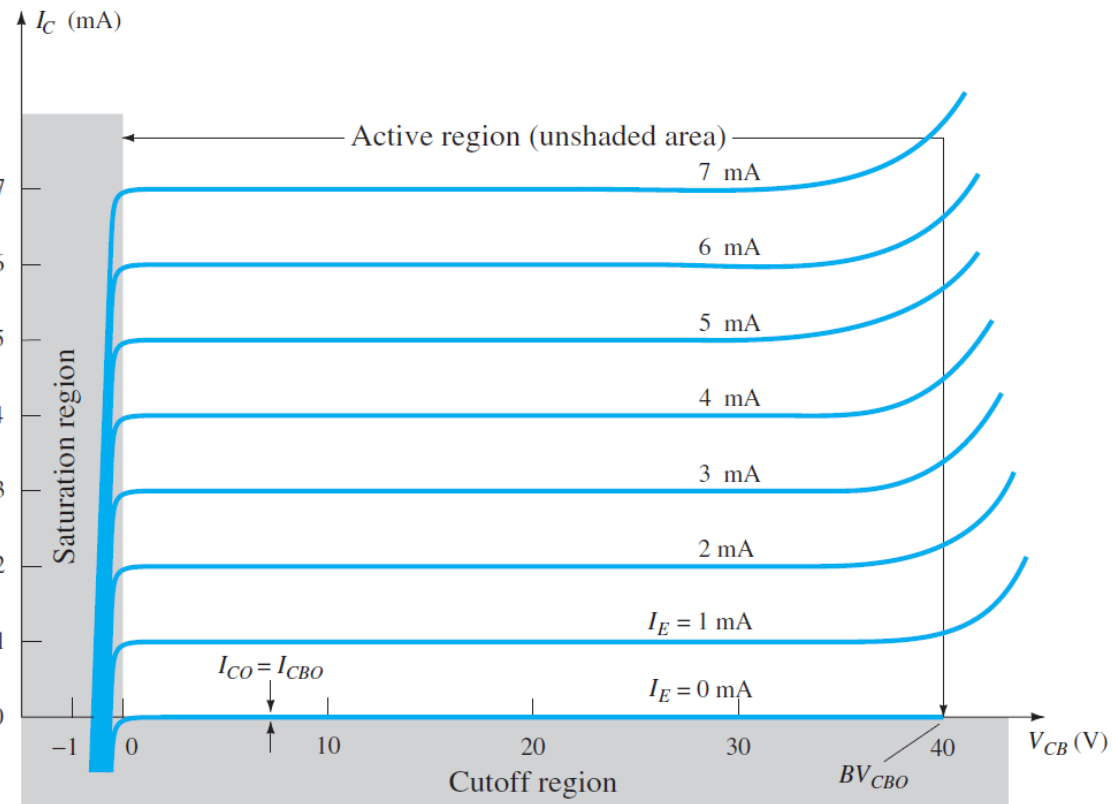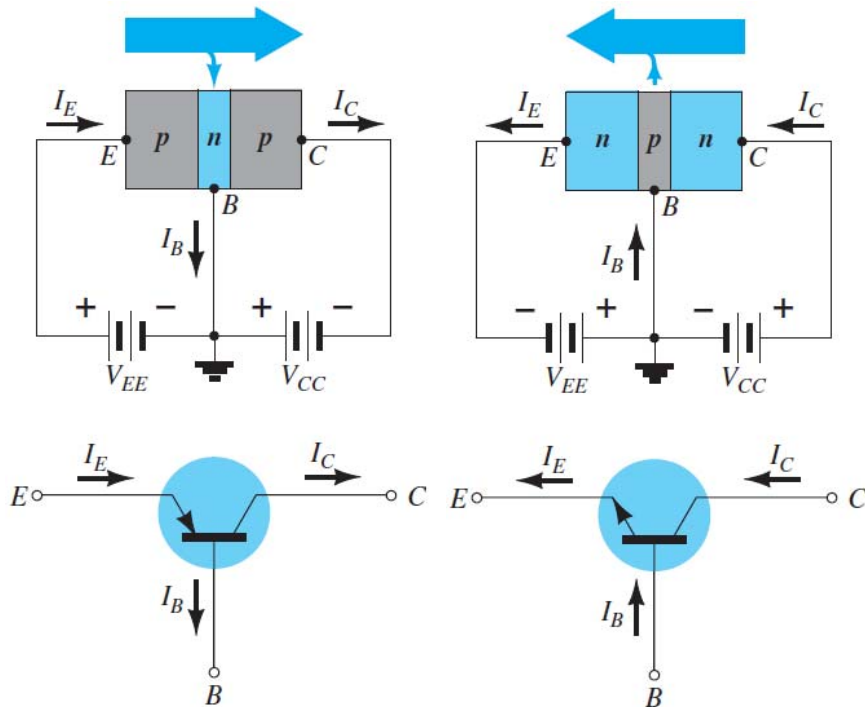Three basic regions of interest →
active, cutoff, and saturation



Common-Base Configuration

Active region →

base-emitter junction is forward-biased
collector-base junction is reverse-biased.

Lower end of active region →




$I_E = 0$, $I_C = I_{CO}$ = microamperes

$I_{CO} = I_{CBO}$ = collector-to-base current emitter leg open

I_E increases above zero →

$I_C \approx I_E$

effect of V_{CB} is negligible.

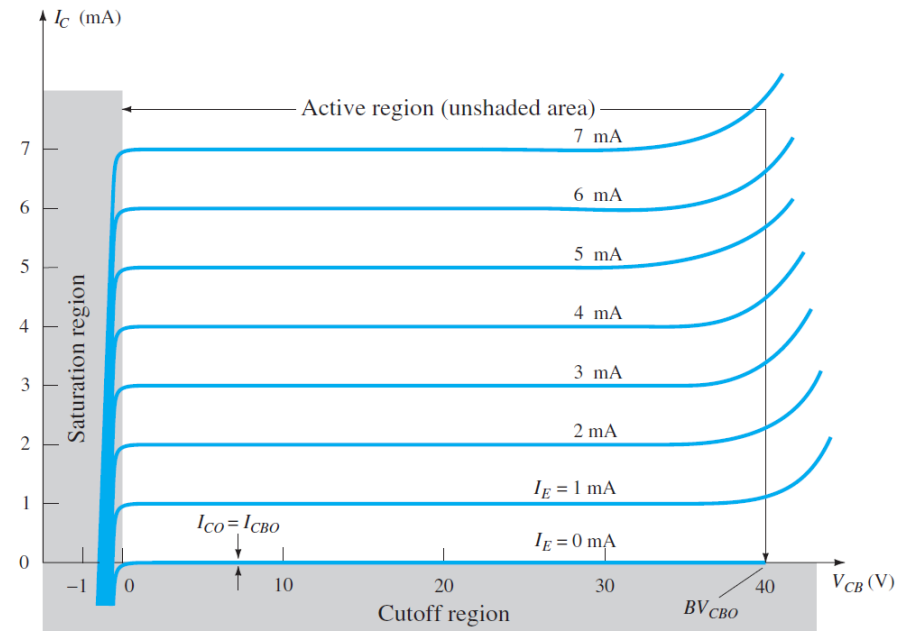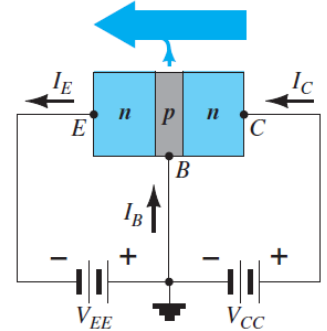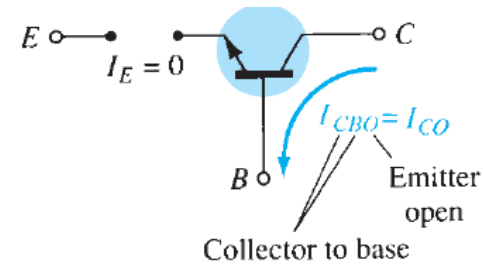

Common-Base Configuration

Cutoff region →

base-emitter and collector-base junctions are both reverse-biased.

$$I_C = 0$$

Saturation region →

base-emitter and collector-base junctions are forward-biased.

