

# **EEE-2103: Electronic Devices and Circuits**

Dept. of Computer Science and Engineering  
University of Dhaka

Prof. Sazzad M.S. Imran, PhD  
Dept. of Electrical and Electronic Engineering  
[sazzadmsi.webnode.com](http://sazzadmsi.webnode.com)

# Silicon-Controlled Rectifier (SCR)





## SCR operation:

4 layers of semiconductor materials.  
 3 junctions-  $J_1$ ,  $J_2$  and  $J_3$ .  
 3 terminals- anode (A), cathode (K) and gate (G).

$+V_{AK} = +ve$  on A and  $-ve$  on K.

G is left unconnected ( $I_G = 0$ )  $\rightarrow$

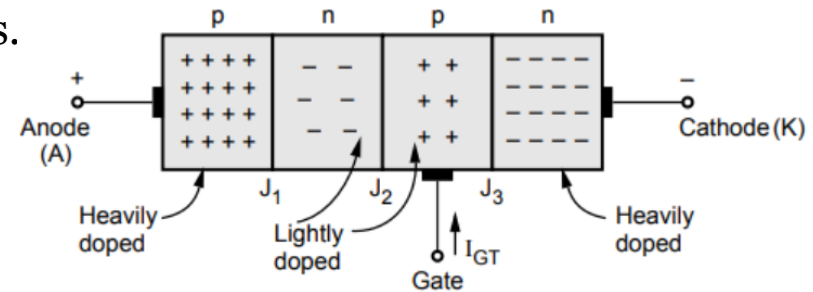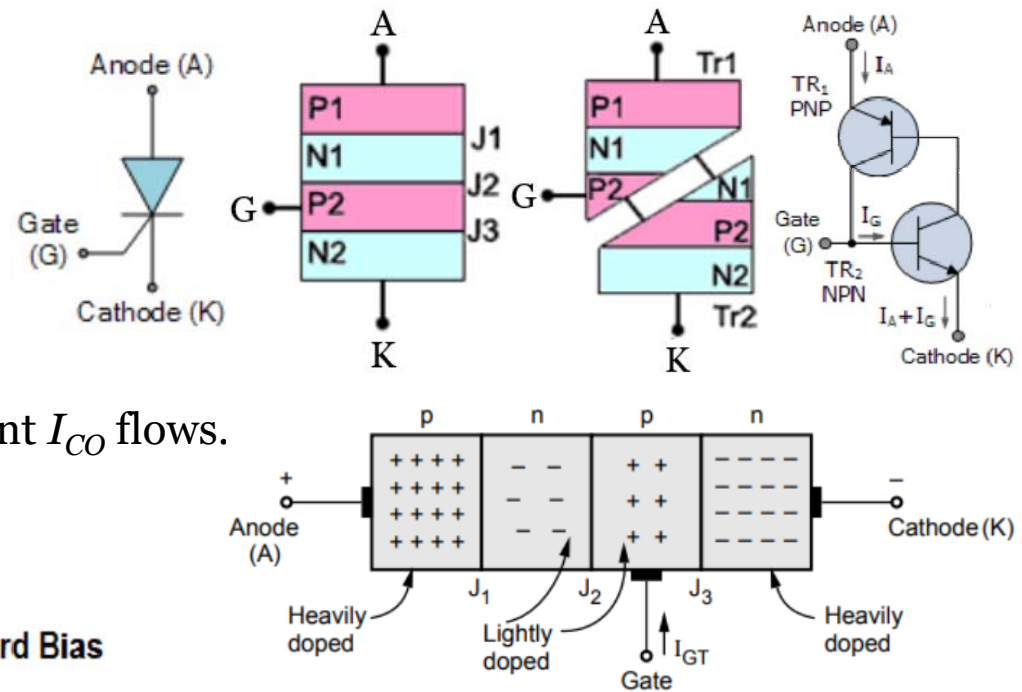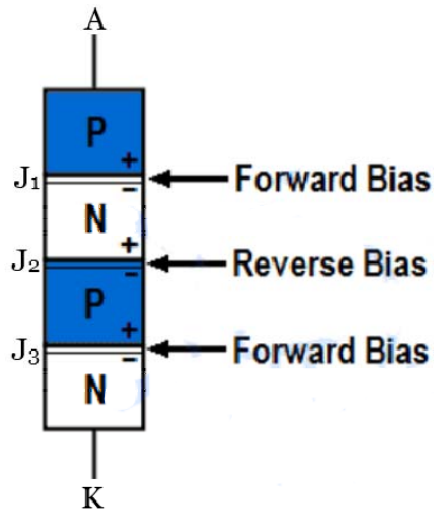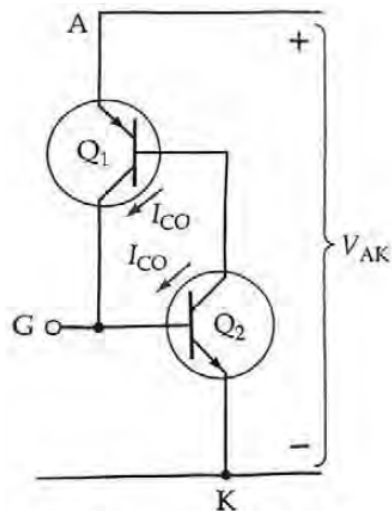$TR_1$  and  $TR_2 = \text{off}$ ; small leakage current  $I_{CO}$  flows.



# Silicon-Controlled Rectifier (SCR)

## SCR operation:

$+V_{AK} = +ve$  on A and  $-ve$  on K.

$-ve$  gate-cathode voltage ( $V_G = -ve$ )  $\rightarrow$

$TR_1$  and  $TR_2 = off$ ; small leakage current flows.

$+V_{AK} = +ve$  on A and  $-ve$  on K.

$+ve$  gate-cathode voltage ( $V_G = +ve$ )  $\rightarrow$

$$I_G = I_{B2} \rightarrow I_{C2}$$


$$I_{C2} = I_{B1} \rightarrow I_{C1}$$

$$I_{C1} = I_{B2} \rightarrow \text{latching}$$

To switch off SCR  $\rightarrow$

no gate control.

$$V_{AK} \approx 0$$

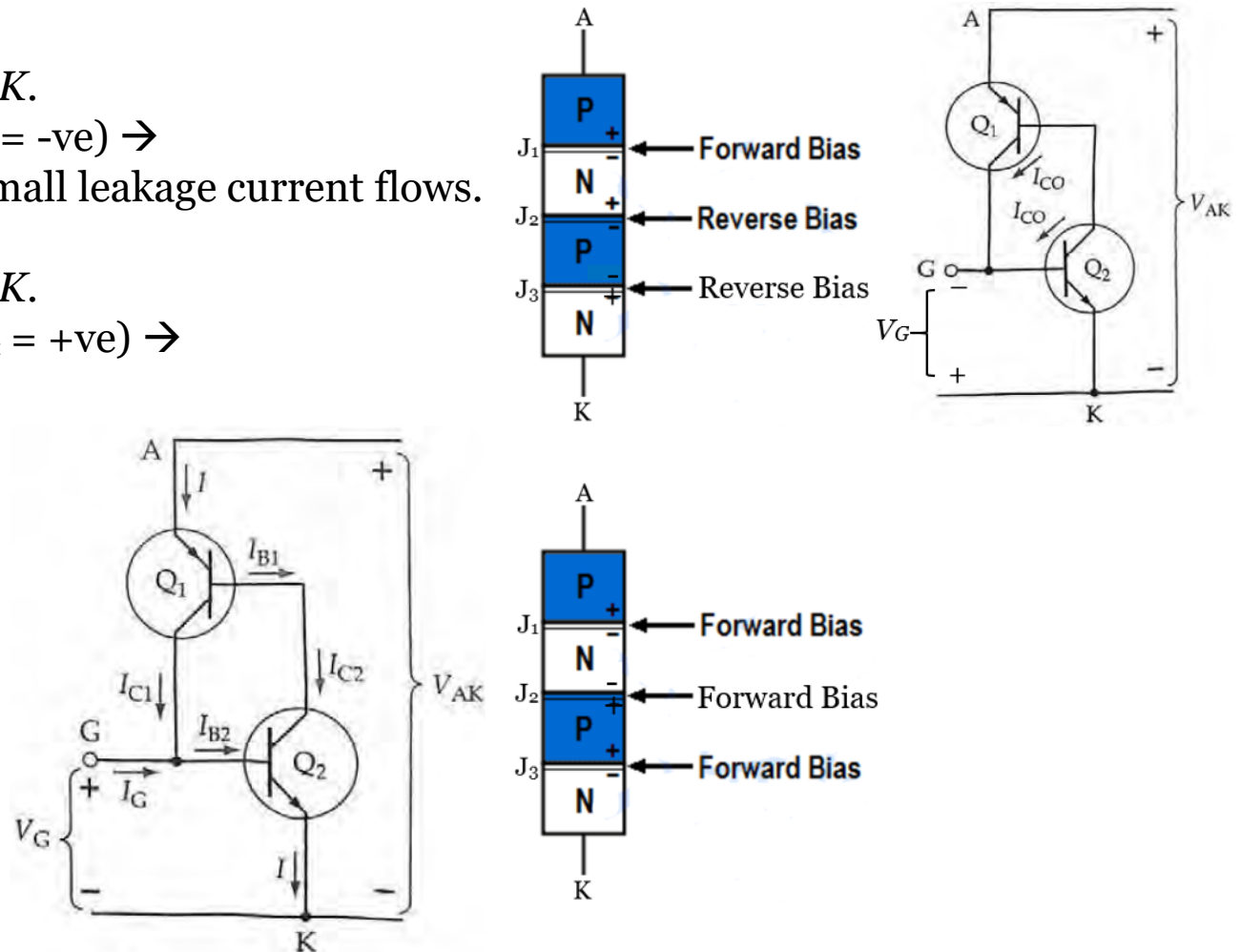

# Silicon-Controlled Rectifier (SCR)

## SCR characteristics:

Reverse bias →

$-V_{AK} = -ve$  on  $A$  and  $+ve$  on  $K$ .

$G$  is left unconnected ( $I_G = 0$ ) →

small  $-V_{AK} \rightarrow$  reverse leakage current  $I_{RX}$  flows.

reverse blocking current  $I_{RX} = 100 \mu A$


$-V_{AK}$  is increased →

$I_{RX}$  remains constant.

reverse breakdown voltage is reached →

$J_1$  and  $J_3$  break down

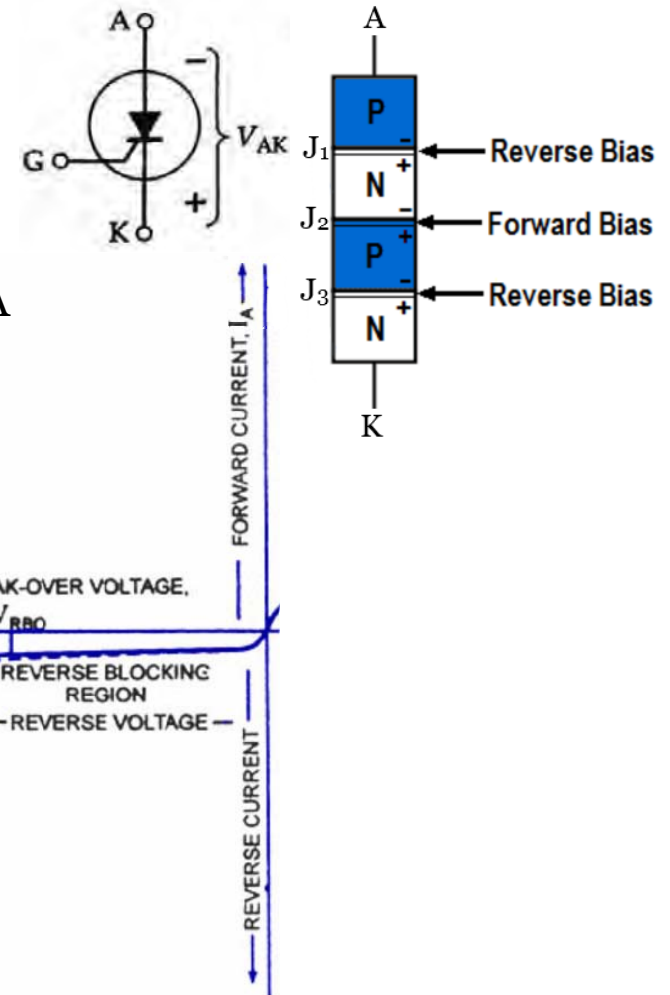reverse current  $I_R$  increases rapidly



# Silicon-Controlled Rectifier (SCR)

## SCR characteristics:

Forward bias →

$+V_{AK} = +ve$  on  $A$  and  $-ve$  on  $K$ .

$G$  is left unconnected ( $I_G = 0$ ) →

small  $+V_{AK} \rightarrow$  forward leakage current  $I_{FX}$  flows.

reverse leakage current at  $J_2$ ,  $I_{FX} = 100 \mu A$

$+V_{AK}$  is increased →

$I_{FX}$  remains constant.

forward breakover voltage  $V_{F(BO)}$  is reached →



$J_2$  breaks down

forward current  $I_F$  increases rapidly

$V_{AK}$  falls rapidly →

$V_{AK} = V_F$  (= forward conduction voltage)

device = forward conduction region

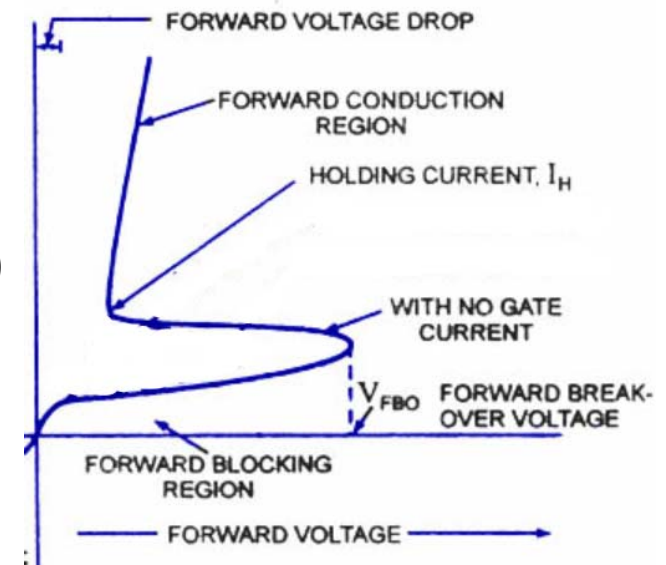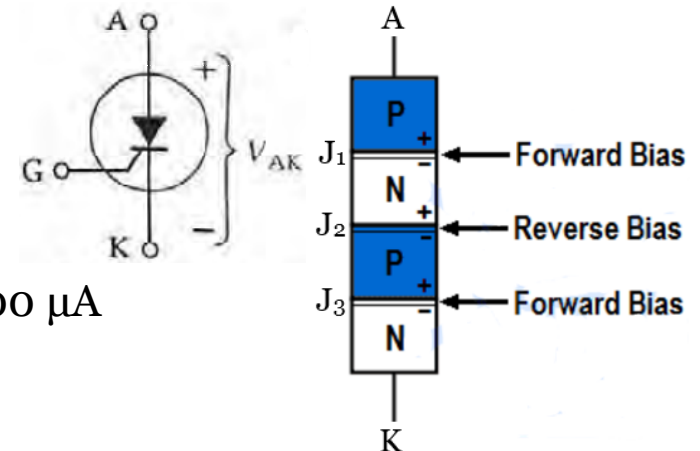

# Silicon-Controlled Rectifier (SCR)

## SCR characteristics:

Forward bias,  $I_G > 0 \rightarrow$

$I_G > I_{B2} \rightarrow Q_2$  becomes on.  
SCR switches on.

Forward blocking region


Forward conduction region

Holding current,  $I_H \rightarrow$  minimum  $I_F$   
that maintains SCR conduction.

To switch SCR off  $\rightarrow$

$$I_F < I_H$$

$$V_{F(on)} = 1.7 \text{ V}$$

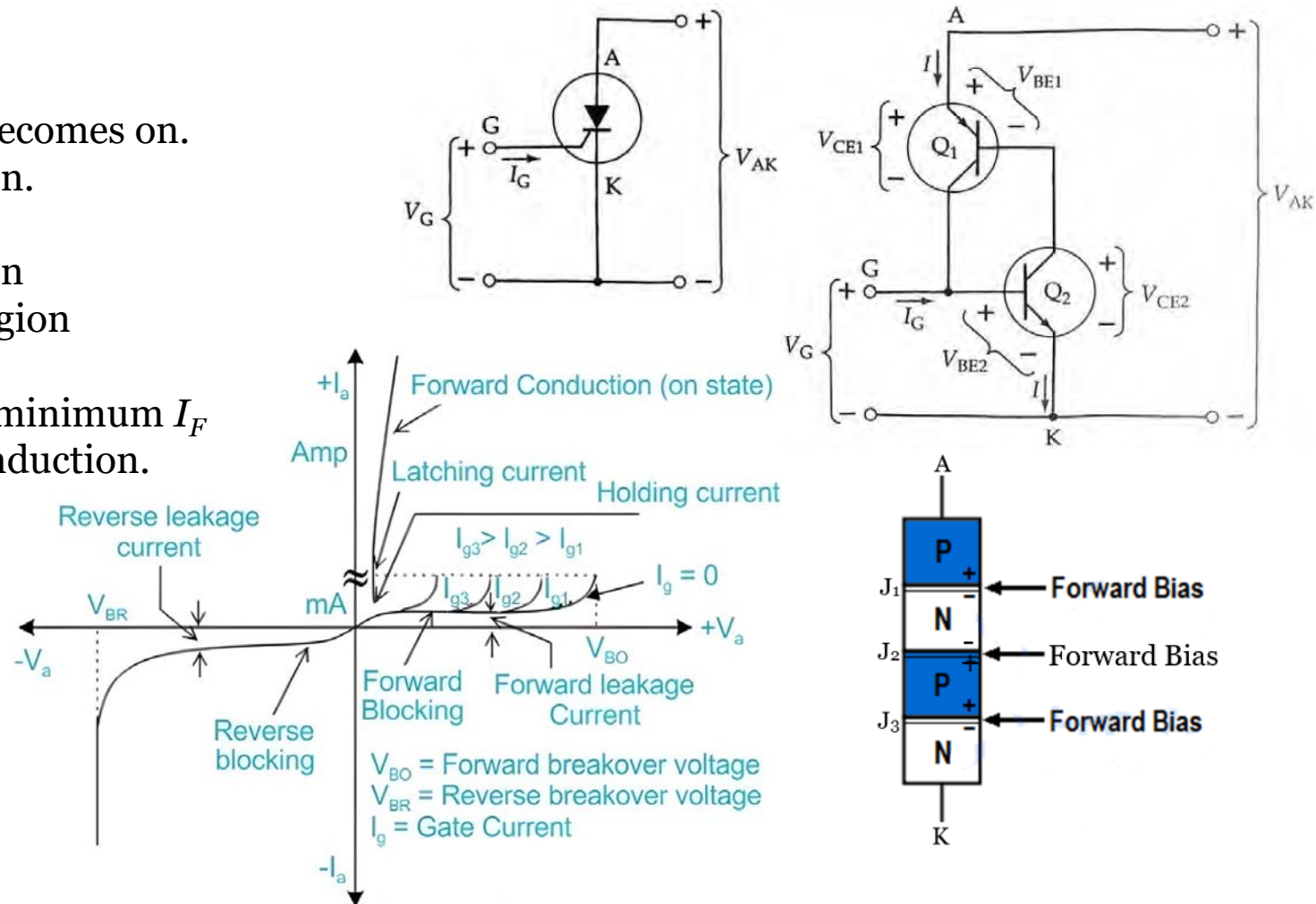

# SCR Control Circuits

## Pulse control:

SCR is triggered on by gate pulse.

Average load power is varied with SCR conduction angle.

SCR is not triggered at  $\alpha = 0^\circ$ .

$V_{AK} \geq V_{TM}$  (= forward on voltage).

SCR will switch off at  $\alpha < 180^\circ$ .

$I_L$  falls below  $I_H$ .

$$V_L = e_s - V_{TM}$$




$$I_L = I_A \approx I_K$$

$$[e_s = \text{supply voltage}]$$

$$[I_K = I_A + I_G, I_G \ll I_A]$$

Instantaneous supply voltage that causes SCR to switch off

$$e_{s(o)} = V_{TM} + I_H R_L$$

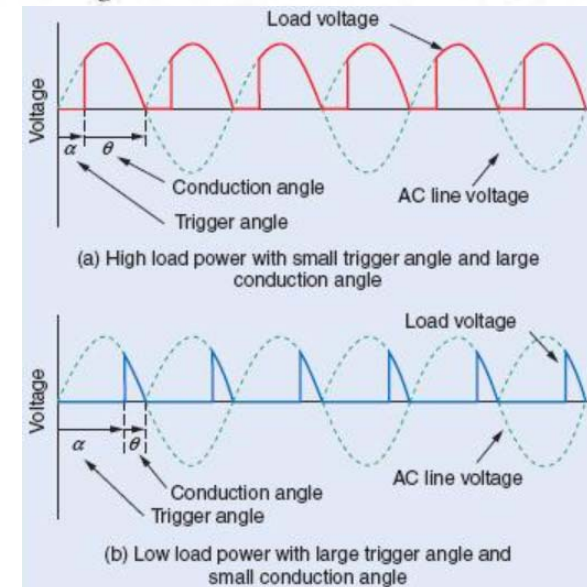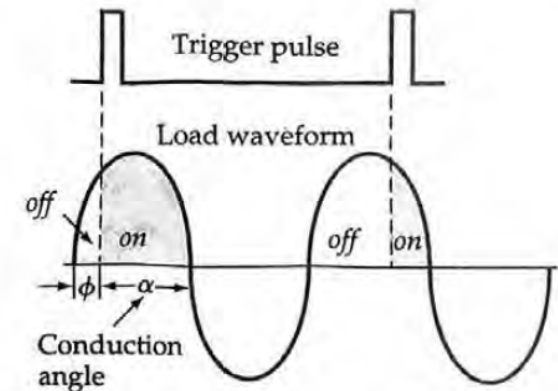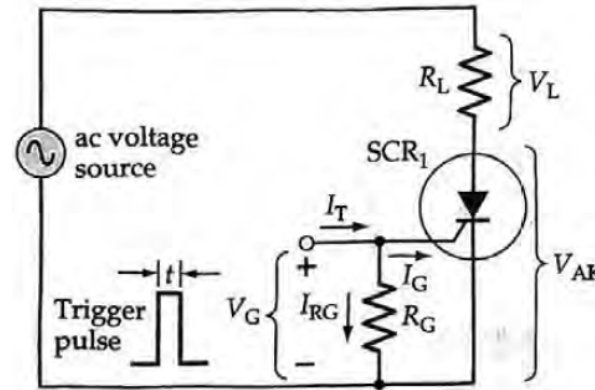

# SCR Control Circuits

90° phase control:

Moving contact is set to top of  $R_2 \rightarrow$   
SCR is triggered on at  $\approx 0^\circ$ .



Moving contact is set to bottom of  $R_2 \rightarrow$   
SCR is triggered on at  $\approx 90^\circ$ .

Moving contact controls  $\alpha \approx 0^\circ \sim 90^\circ$ .

$D_1$  protects SCR gate from  $-V_G$  during -ve half-cycle of ac supply.

Instantaneous triggering voltage at switch-on


$$V_T = V_{D1} + V_G$$

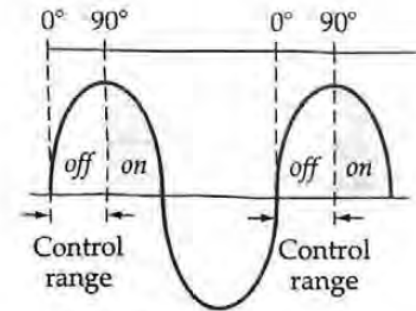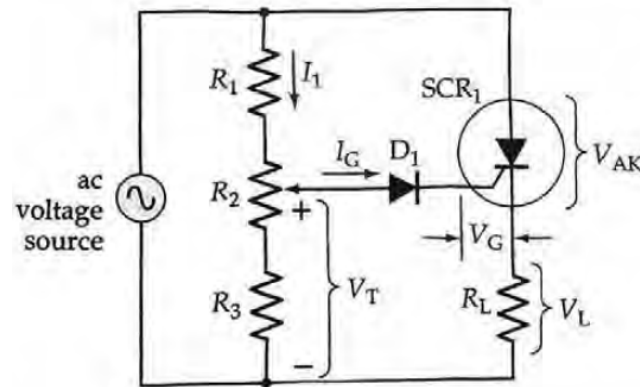



# SCR Control Circuits

90° phase control (full-wave-rectified):

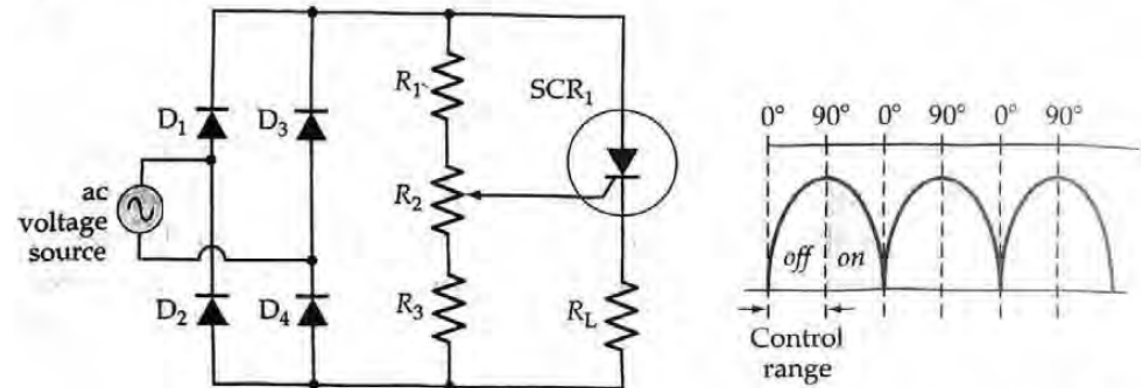

90° full-wave phase control:

+ve half-cycle  $\rightarrow$


$D_2$  is forward-biased.

Current flows through  $R_2, R_3$  and  $R_4$

-ve half-cycle  $\rightarrow$

$D_1$  is forward-biased.

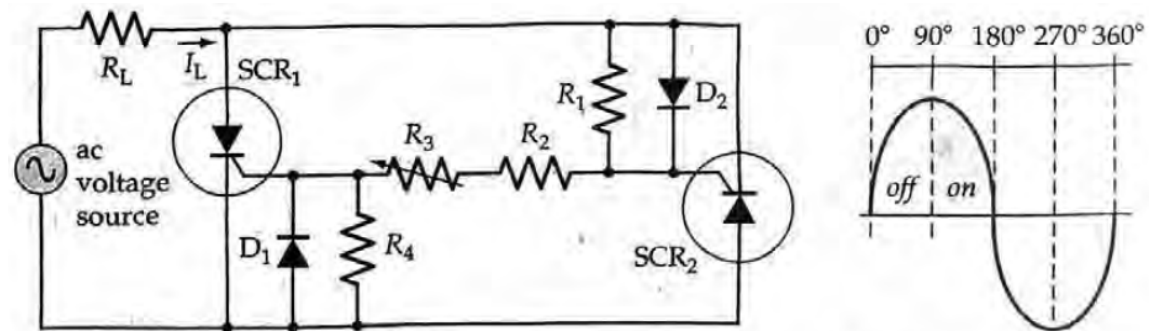Current flows through  $R_1, R_2$  and  $R_3$



$$R_1 = R_4 \rightarrow \alpha_1 = \alpha_2$$

# SCR Control Circuits

## Problem-41:

The SCR in Fig. 41 is to be triggered on between  $5^\circ$  and  $90^\circ$  during the positive half-cycle of the 30 V supply. The gate triggering current and voltage are  $200\ \mu\text{A}$  and  $0.8\ \text{V}$ . Determine suitable resistance values for  $R_1$ ,  $R_2$  and  $R_3$ . Also, determine the SCR anode-cathode voltage at the instant of switch-on when the moving contact of potentiometer  $R_2$  is set to (a) its center position and (b) its zero (bottom) position.

Peak supply voltage,  $V_{s(pk)} = 1.414 \times V_s = 1.414 \times 30 = 42.4\ \text{V}$

At  $5^\circ$ ,  $e_s = V_{s(pk)} \sin 5^\circ = 42.4 \times \sin 5^\circ \approx 3.7\ \text{V}$

At  $90^\circ$ ,  $e_s = V_{s(pk)} = 42.4\ \text{V}$

Triggering voltage at switch-on,  $V_T = V_{D1} + V_G = 0.7 + 0.8 = 1.5\ \text{V}$

To trigger at  $e_s = 3.7\ \text{V}$ ,  $R_2$  moving contact is at top.


$$V_{R2} + V_{R3} = V_T = 1.5\ \text{V}$$

$$V_{R1} = e_s - V_T = 3.7 - 1.5 = 2.2\ \text{V}$$

Select  $I_{1(min)} = 1\ \text{mA}$  ( $\gg I_G = 200\ \mu\text{A}$ )

$$R_1 = V_{R1} / I_1 = 2.2 / 1 \times 10^{-3} = 2.2\ \text{k}\Omega$$
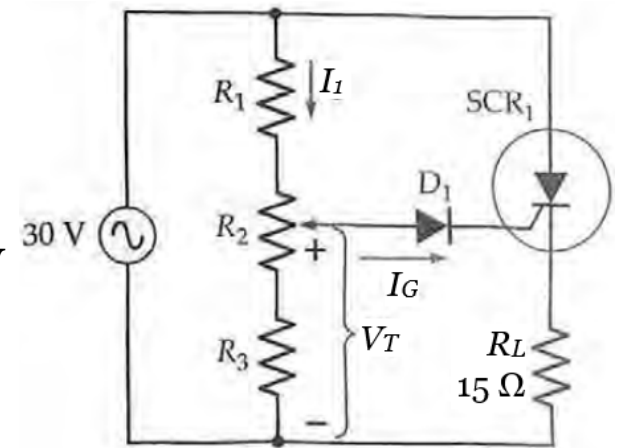
$$R_2 + R_3 = V_T / I_1 = 1.5 / 1 \times 10^{-3} = 1.5\ \text{k}\Omega$$



# SCR Control Circuits

## Problem-41:

To trigger at  $e_s = 42.4$  V,  $R_2$  moving contact is at bottom.

$$V_{R_3} = V_T = 1.5 \text{ V}$$

$$I_1 = \frac{e_s}{R_1 + R_2 + R_3} = \frac{42.4}{2.2 \times 10^3 + 1.5 \times 10^3} \approx 11.5 \text{ mA}$$

$$R_3 = V_T / I_1 = 1.5 / 11.5 \times 10^{-3} = 130 \Omega \text{ (use } 120 \Omega \text{ standard value)}$$

$$R_2 = (R_2 + R_3) - R_3 = 1.5 \times 10^3 - 120 = 1.38 \text{ k}\Omega$$

(use 1.5 k $\Omega$  standard value)

(a) SCR will trigger when  $V_T = 1.5$  V ( $R_2$  contact at center)

$$V_{AK} = \frac{V_T(R_1 + R_2 + R_3)}{R_3 + 0.5R_2} = \frac{1.5(2.2 \times 10^3 + 1.5 \times 10^3 + 120)}{120 + \frac{1}{2}(1.5 \times 10^3)} = 6.6 \text{ V}$$

(b) With  $R_2$  contact at zero

$$V_{AK} = \frac{V_T(R_1 + R_2 + R_3)}{R_3} = \frac{1.5(2.2 \times 10^3 + 1.5 \times 10^3 + 120)}{120} = 47.85 \text{ V}$$

Because  $V_{s(pk)} = 42.4$  V, SCR will not trigger with  $R_2$  at zero position.

