

EEE-2103: Electronic Devices and Circuits

Dept. of Computer Science and Engineering
University of Dhaka

Prof. Sazzad M.S. Imran, PhD
Dept. of Electrical and Electronic Engineering
sazzadmsi.webnode.com

Fixed-Bias Configuration of JFET

Coupling capacitors \rightarrow open circuits for dc analysis and short circuits for ac analysis.


$R_G \rightarrow$ to ensure that V_i appears at input for ac analysis.

For dc analysis \rightarrow $I_G \approx 0 \text{ A}$
 $V_{RG} = I_G R_G = (0) R_G = 0 \text{ V}$

$$V_{GS} = -V_{GG}$$

I_D is controlled by Shockley's equation \rightarrow
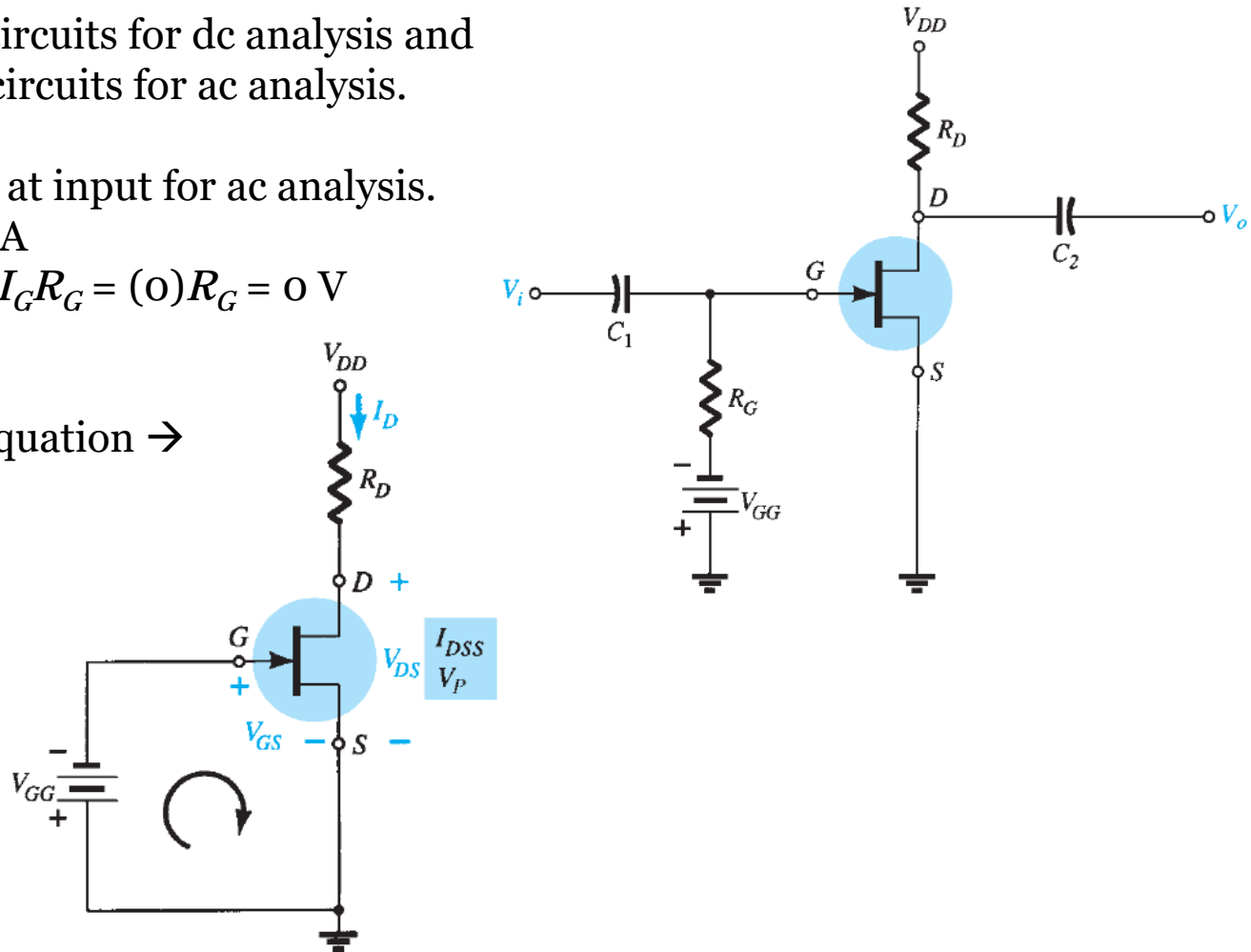
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



Fixed-Bias Configuration of JFET

Quiescent or operating point $\rightarrow V_{GS} = -V_{GG}$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$+V_{DS} + I_D R_D - V_{DD} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$



$$V_S = 0 \text{ V}$$

$$V_{DS} = V_D - V_S$$

$$V_D = V_{DS} + V_S = V_{DS} + 0 \text{ V} = V_{DS}$$

$$V_{GS} = V_G - V_S$$
  
$$V_G = V_{GS} + V_S = V_{GS} + 0 \text{ V} = V_{GS}$$



Fixed-Bias Configuration of JFET

Problem-38:

Determine the following for the network of Fig. 38.

a) V_{GSQ} . b) I_{DQ} . c) V_{DS} . d) V_D . e) V_G . f) V_S .

Draw the resulting Shockley curve and show the Q -point of biased circuit.

a) $V_{GSQ} = -V_{GG} = -2 \text{ V}$



b) $I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 10 \times 10^{-3} \left(1 - \frac{-2}{-8}\right)^2 = 5.625 \text{ mA}$

c) $V_{DS} = V_{DD} - I_D R_D = 16 - (5.625 \times 10^{-3})(2 \times 10^3) = 4.75 \text{ V}$

d) $V_D = V_{DS} = 4.75 \text{ V}$

e) $V_G = V_{GS} = -2 \text{ V}$

f) $V_S = 0 \text{ V}$

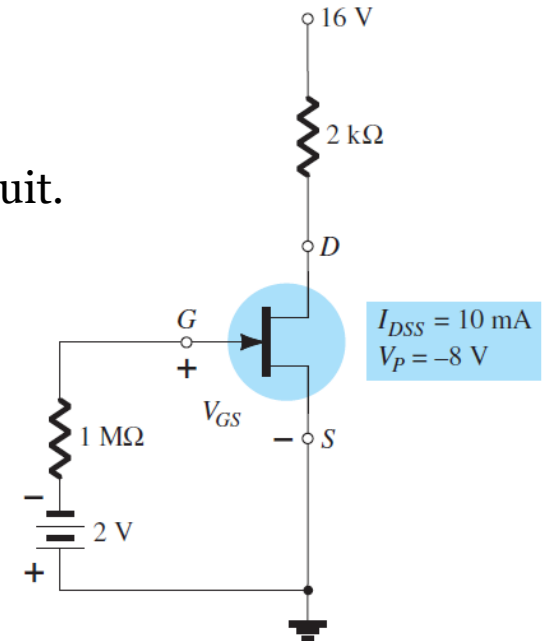 

Self-Bias Configuration of JFET

dc analysis \rightarrow capacitors are replaced by open circuits
 R_G is replaced by short-circuit equivalent since $I_G = 0$ A.

$$I_S = I_D$$


$$V_{RS} = I_D R_S$$

$$-V_{GS} - V_{RS} = 0$$

$$V_{GS} = -V_{RS} = -I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = I_{DSS} \left(1 - \frac{-I_D R_S}{V_P} \right)^2$$
 
$$= I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2$$



Self-Bias Configuration of JFET

Quiescent or operating point \rightarrow

1st point $\rightarrow I_D = 0 \text{ A}$, $V_{GS} = -I_D R_S = (0)R_S = 0 \text{ V}$.

2nd point $\rightarrow I_D = I_{DSS}/2$, $V_{GS} = -I_D R_S = -I_{DSS} R_S/2$.

$$V_{RS} + V_{DS} + V_{RD} - V_{DD} = 0$$

$$V_{DS} = V_{DD} - V_{RS} - V_{RD} = V_{DD} - I_S R_S - I_D R_D$$




$$I_D = I_S$$

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$V_S = I_D R_S$$

$$V_G = 0 \text{ V}$$

$$V_D = V_{DS} + V_S = V_{DD} - V_{RD}$$

   

Self-Bias Configuration of JFET

Problem-39:



Determine the following for the network of Fig. 39.

a) V_{GSQ} . b) I_{DQ} . c) V_{DS} . d) V_S . e) V_G . f) V_D .

  a) $V_{GS} = -I_D R_S$

Choosing $I_D = 4 \text{ mA}$, $V_{GS} = -(4 \times 10^{-3})(1 \times 10^3) = -4 \text{ V}$


Choosing $I_D = 8 \text{ mA}$, $V_{GS} = -(8 \times 10^{-3})(1 \times 10^3) = -8 \text{ V}$



Self-Bias Configuration of JFET

Problem-39:

 a) Choosing $V_{GS} = V_P/2 = -3 \text{ V}$, $I_D = I_{DSS}/4 = 8/4 = 2 \text{ mA}$



$$V_{GSQ} = 2.6 \text{ V}$$

b) $I_{DQ} = 2.6 \text{ mA}$

Self-Bias Configuration of JFET


Problem-39:

c) $V_{DS} = V_{DD} - I_D(R_S + R_D) = 20 - (2.6 \times 10^{-3})(1 \times 10^3 + 3.3 \times 10^3) = 8.82 \text{ V}$

d) $V_S = I_D R_S = (2.6 \times 10^{-3})(1 \times 10^3) = 2.6 \text{ V}$

e) $V_G = 0 \text{ V}$

 f) $V_D = V_{DS} + V_S = 8.82 + 2.6 = 11.42 \text{ V}$



Voltage-Divider Biasing of JFET

Coupling capacitors \rightarrow open circuits for dc analysis and short circuits for ac analysis.

$$I_G = 0 \text{ A}, I_{R1} = I_{R2}, V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

Applying Kirchhoff's voltage law

$$V_G - V_{GS} - V_{RS} = 0$$

$$V_{GS} = V_G - V_{RS}$$

Substituting $V_{RS} = I_S R_S = I_D R_S$,

$$V_{GS} = V_G - I_D R_S$$


1st point $\rightarrow I_D = 0 \text{ mA}$

$$V_{GS} = V_G - I_D R_S = V_G - (0) R_S = V_G$$

2nd point $\rightarrow V_{GS} = 0 \text{ V}$

$$V_{GS} = V_G - I_D R_S = 0 \text{ V}$$

$$I_D = V_G / R_S$$

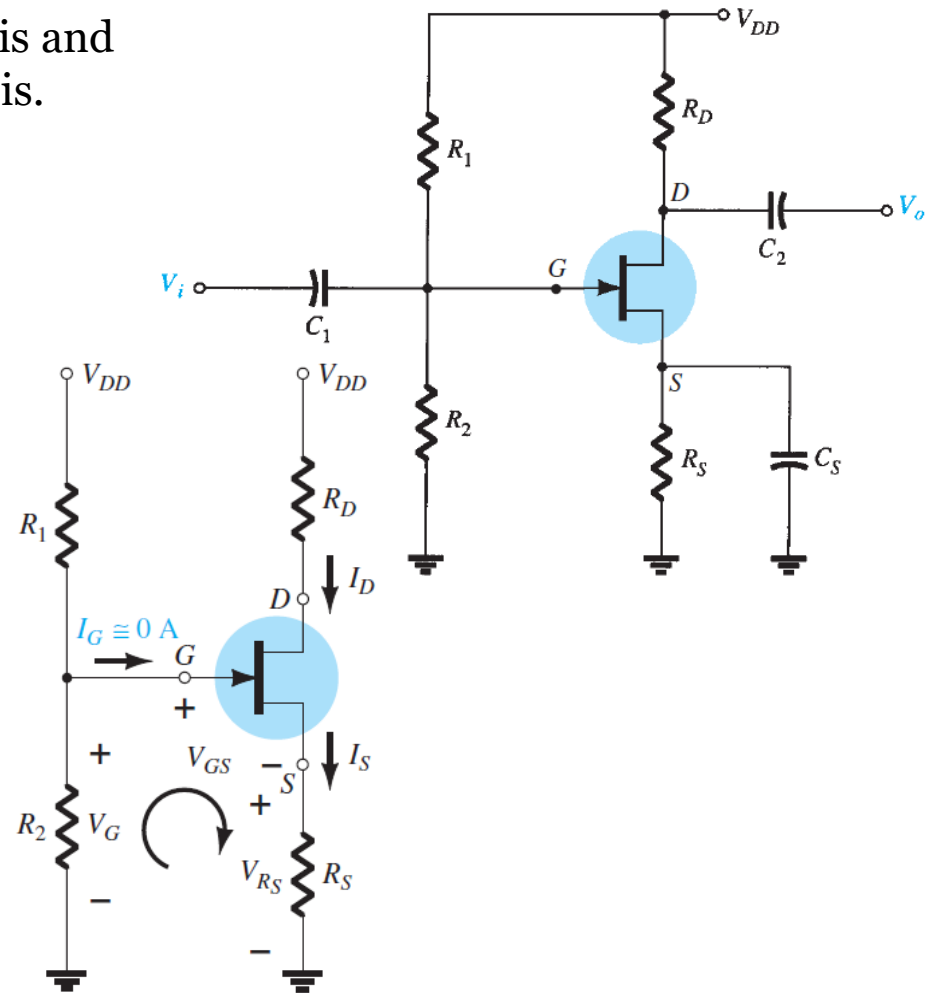

Voltage-Divider Biasing of JFET

$$I_D = 0 \text{ mA}, V_{GS} = V_G$$

$$V_{GS} = 0 \text{ V}, I_D = V_G / R_S$$



R_S increases \rightarrow lower I_{DQ}
decline V_{GS} .

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$
  
$$I_{R_1} = I_{R_2} = \frac{V_{DD}}{R_1 + R_2}$$



Voltage-Divider Biasing of JFET

Problem-40:

Determine the following for the network of Fig. 40.

a) I_{DQ} and V_{GSQ} . b) V_D . c) V_S . d) V_{DS} . e) V_{DG} .

a) For transfer characteristics,

$$I_D = I_{DSS}/4 = 8/4 = 2 \text{ mA},$$

$$V_{GS} = V_P/2 = -4/2 = -2 \text{ V}.$$

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2} = \frac{(270 \times 10^3)(16)}{2.1 \times 10^6 + 0.27 \times 10^3} = 1.82 \text{ V}$$



$$V_{GS} = V_G - I_D R_S = 1.82 - I_D(1.5 \times 10^3)$$

$$I_D = 0 \text{ mA}, V_{GS} = +1.82 \text{ V}$$

$$V_{GS} = 0 \text{ V}, I_D = 1.82 / (1.5 \times 10^3) = 1.21 \text{ mA}$$

$$I_{DQ} = 2.4 \text{ mA}$$

$$V_{GSQ} = -1.8 \text{ V}$$

  

Voltage-Divider Biasing of JFET

Problem-40:

b) $V_D = V_{DD} - I_D R_D = 16 - (2.4 \times 10^{-3})(2.4 \times 10^3) = 10.24 \text{ V}$

c) $V_S = I_D R_S = (2.4 \times 10^{-3})(1.5 \times 10^3) = 3.6 \text{ V}$

d) $V_{DS} = V_{DD} - I_D(R_D + R_S)$
 $= 16 - (2.4 \times 10^{-3})(2.4 \times 10^3 + 1.5 \times 10^3) = 6.64 \text{ V}$

e) $V_{DG} = V_D - V_G = 10.24 - 1.82 = 8.42 \text{ V}$

